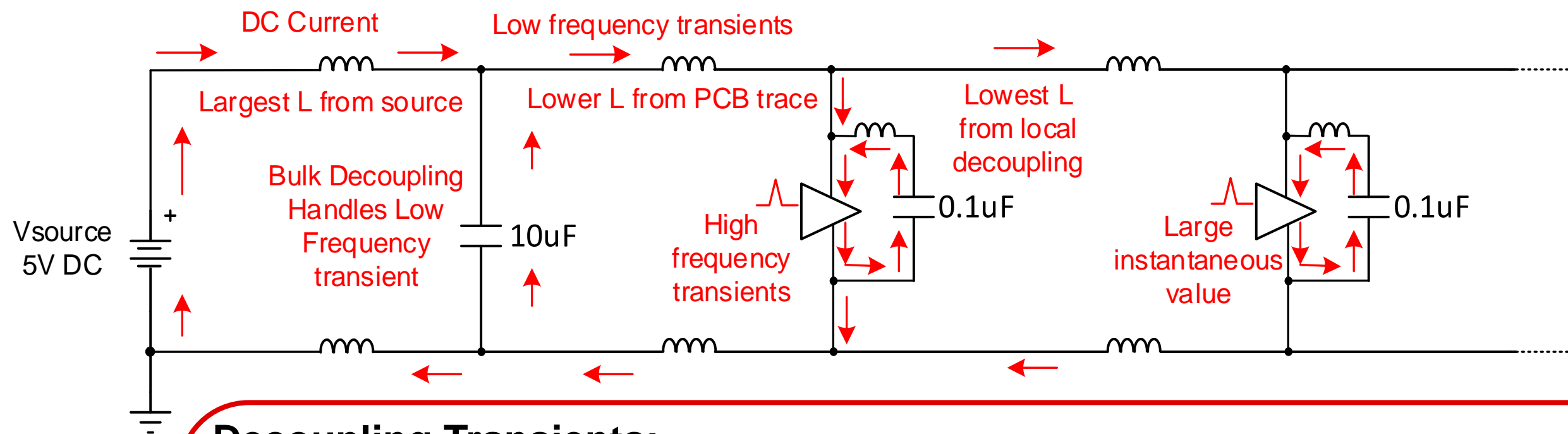


Decoupling capacitors

TI Precision Labs – ADCs

Created and Presented by Art Kay


Decoupling from a Transient Perspective



Decoupling Transients:


- Local decoupling provides high frequency transient current
- Instantaneous transient current from device can be high
- Bulk decoupling provides low frequency current
- The source has highest inductance, PCB power traces have lower inductance, and local decoupling has lowest inductance
- Decoupling minimizes noise local to device and minimizes the impact on other devices sharing the power bus

 Decoupling from an AC Impedance Perspective





Impedance Seen by Device:

 - High impedance at DC
- *Ideally* would have zero impedance at high frequency to short out high frequency transients
- Practical decoupling will be low at high frequency but will begin to increase from parasitic inductance.
- Practical decoupling may have multiple resonant peaks






Model of a practical capacitor

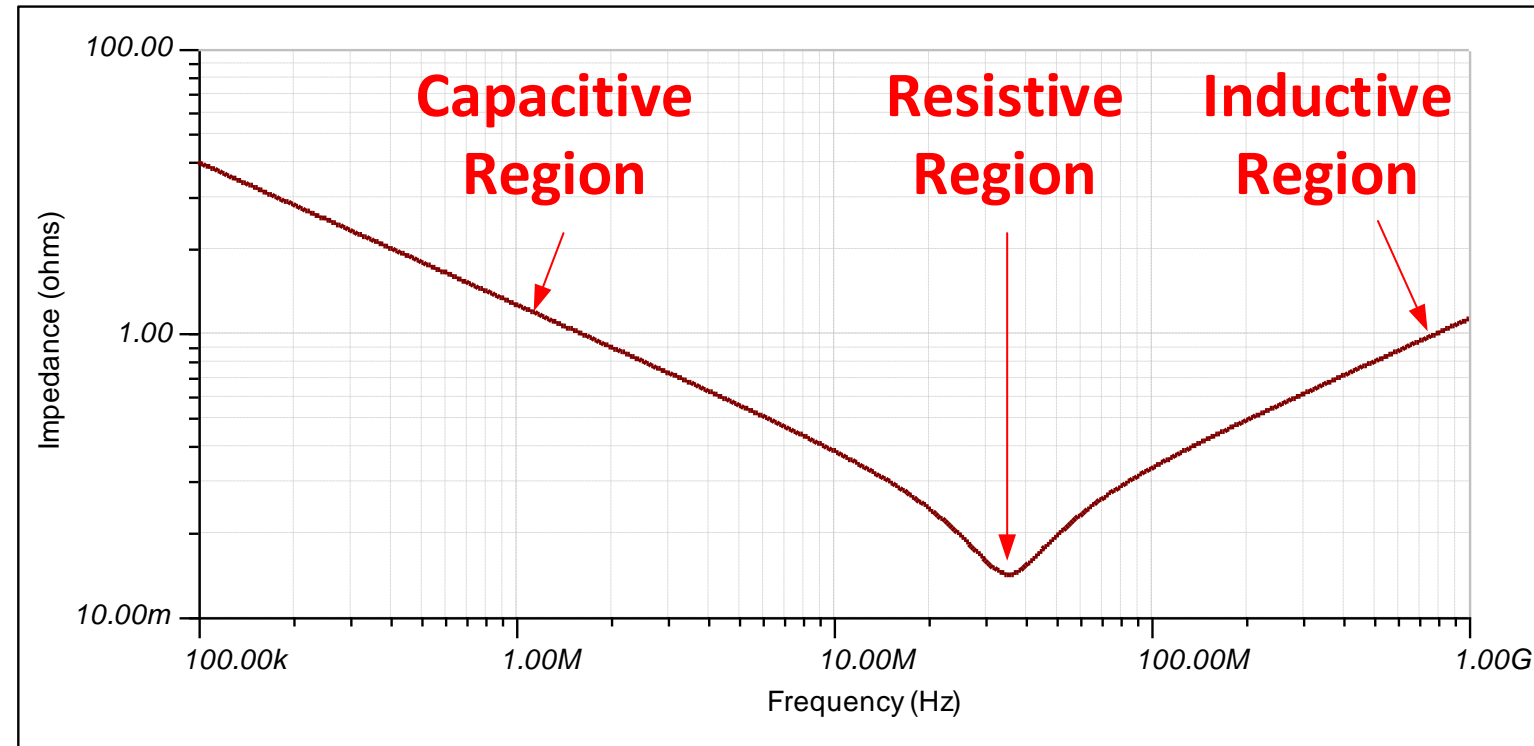 

Practical impedance of Capacitor:

- ESR – parasitic resistance of capacitor
- ESL – parasitic inductance of capacitor
- Practical capacitor acts like capacitor at low frequency and like an inductor at high frequency
- Values shown in this example are typical for a X7R decoupling capacitor
- More accurate models provided by capacitor manufacture.

 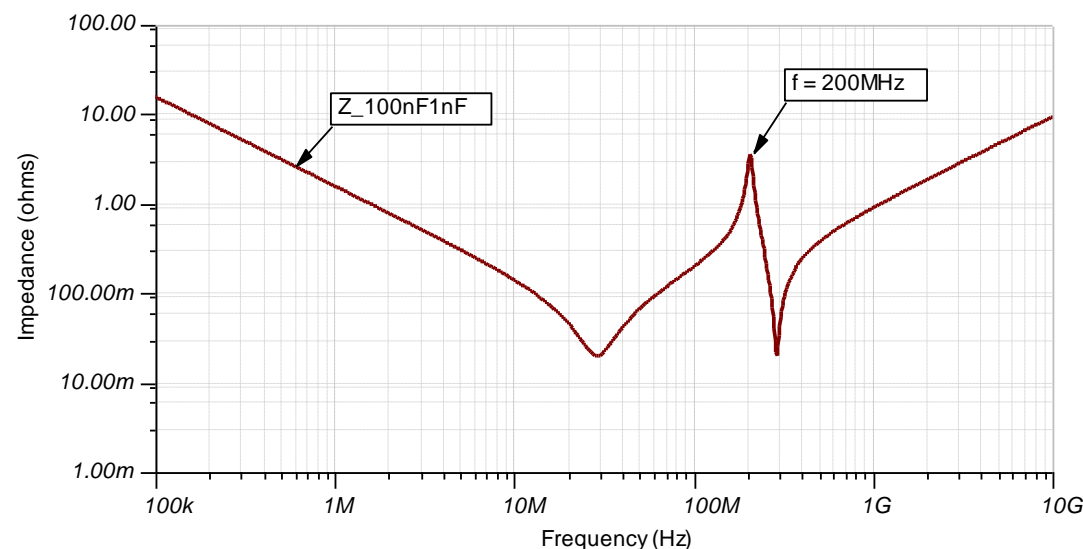
 
Resonance from Different Decoupling Capacitors



Don't use two different capacitor values for “better” high frequency bypass

- The practice of using two different parallel capacitors was developed 1970's for through-hole capacitors. It doesn't apply to modern surface mount ceramic
- ESL is relatively independent of capacitance value
 - e.g. ESL for a 100pF, 1000pF, and 10,000pF (25V, 0603, X7R) is approximately the same (ESL \approx 200pH GRM033R71E103ME14, GRM033R71E102ME14, GRM033R71E101ME14)
- Using two different parallel capacitors can create a resonance

Multiple Same Value Decoupling

 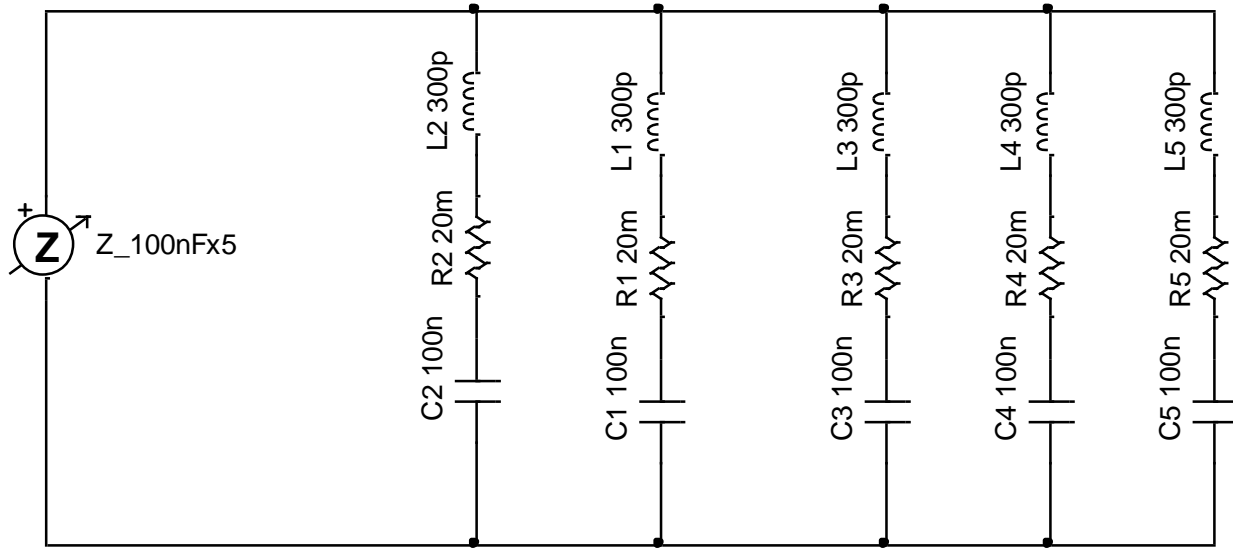


Using Multiple Same Type / Value Decoupling Capacitors

- Total impedance is divided by the number of capacitors
 - The example shows five capacitors in parallel ($Z_{total} = Z_c/5$)
- No resonance in impedance -- all capacitors are the same


PCB Design for good decoupling

- **Main objective:** reduce the parasitic inductances from traces and vias.
- Use short wide traces or polygons
- Use multiple vias (or larger via) for plane connections if possible
- Thin dielectric spacing between top layer and plane reduce via inductance
- Use low ESL capacitor


Schematic Design

 

Layout

 

Circuit including parasitics

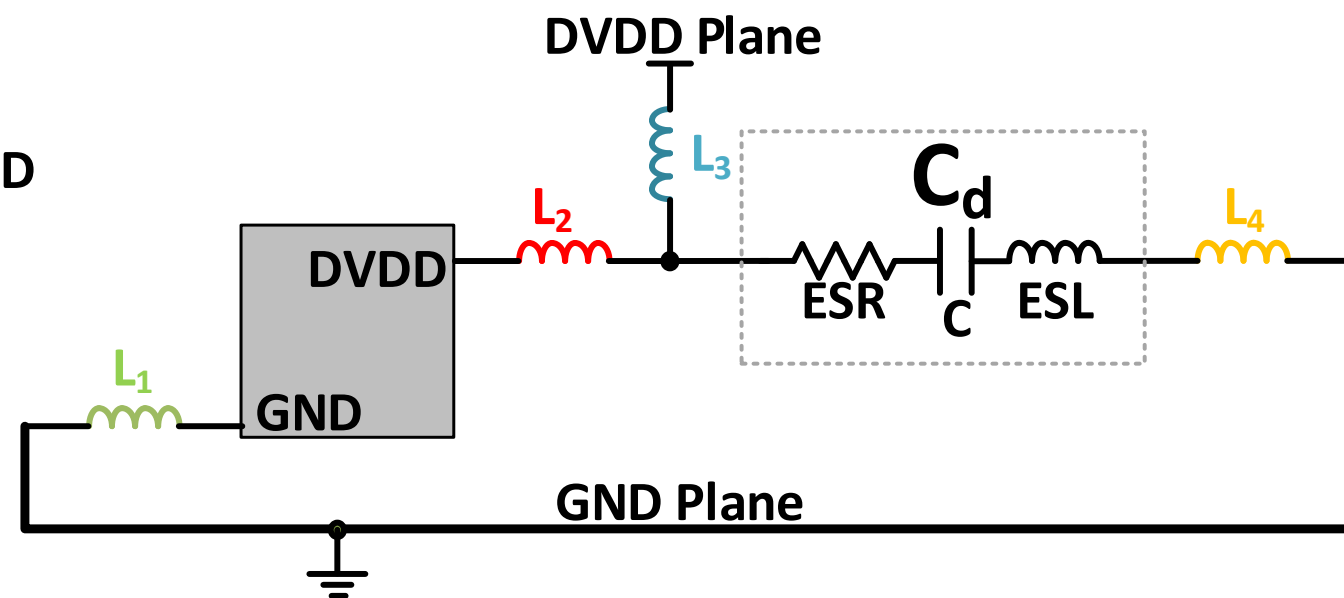


via inductance

Via inductance		
Drill hole (mil)	h - Distance to Plane (mil)	Inductance - FR4
12	9	0.0959nH
12	62	1.26782nH
16	9	0.08273nH
16	62	1.17729nH
20	9	0.07253nH
20	62	1.10706nH

Note 1: 9 mil is typical pre-preg thickness, 62 mil is typical two layer board thickness.
Note 2: 12 mil is typical minimum drilled via hole size.

Via Inductance

 - Reducing dielectric thickness (h) significantly reduces inductance
- Using larger vias also helps incrementally
- Multiple vias are parallel inductors, so two similar vias will cut the inductance in half




Trace inductance


Trace inductance			
Length (mil)	Width (mil)	h - Distance to Plane (mil)	Inductance
100	8	9	0.9814n
100	8	62	1.960n
100	12	9	0.8065n
100	12	62	1.785n
100	20	9	0.5735n
100	20	62	1.552n
1000	20	9	5.735n
1000	20	62	15.52n

Trace Inductance

 
- Increasing width decreases inductance
- Decreasing the length decreases inductance
- Reducing dielectric thickness reduces inductance



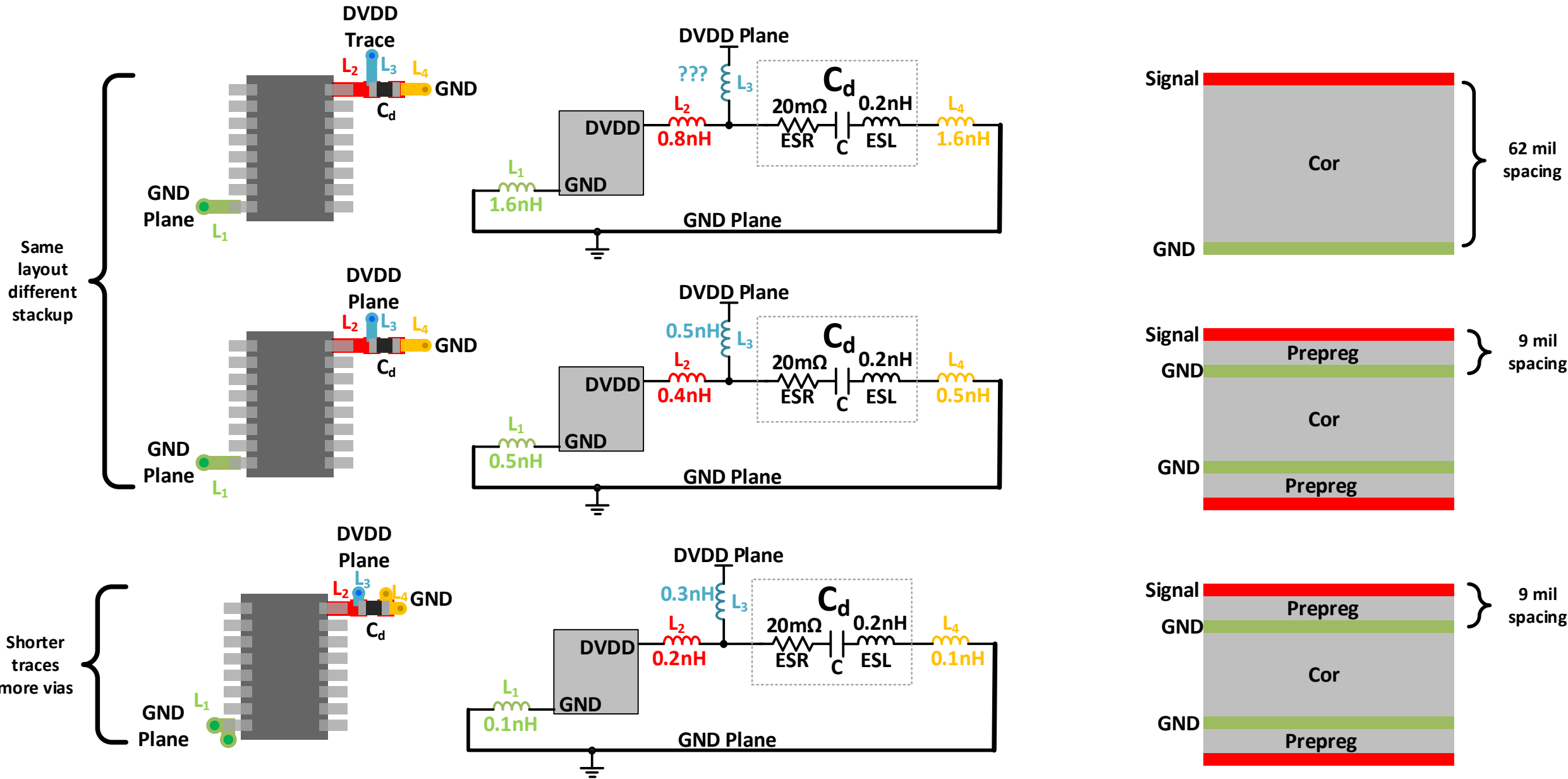Comparison of parasitic inductance and ESL




 Can return current flow through the power plane?





Can return current flow through the power plane?

 - It seems counter intuitive that return current can flow through the power plane, but it can.
- The next two slides will show how current flows in the GND or power plane for a CMOS gate depending on which plane is adjacent to the signal path.




Does the return current really flow here?

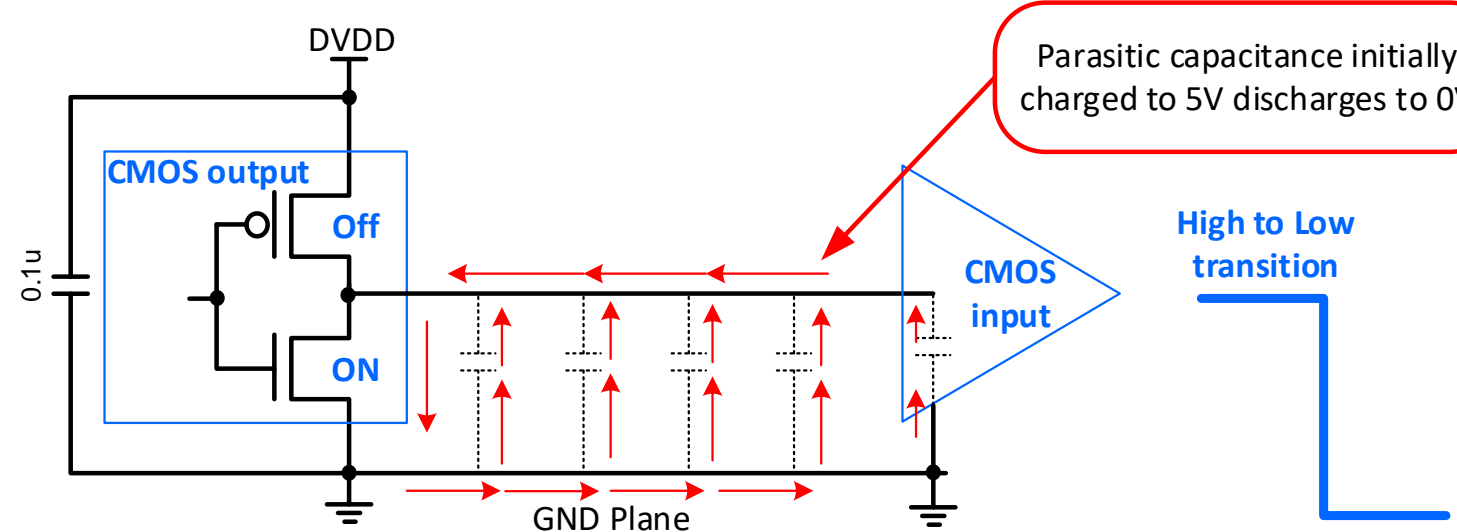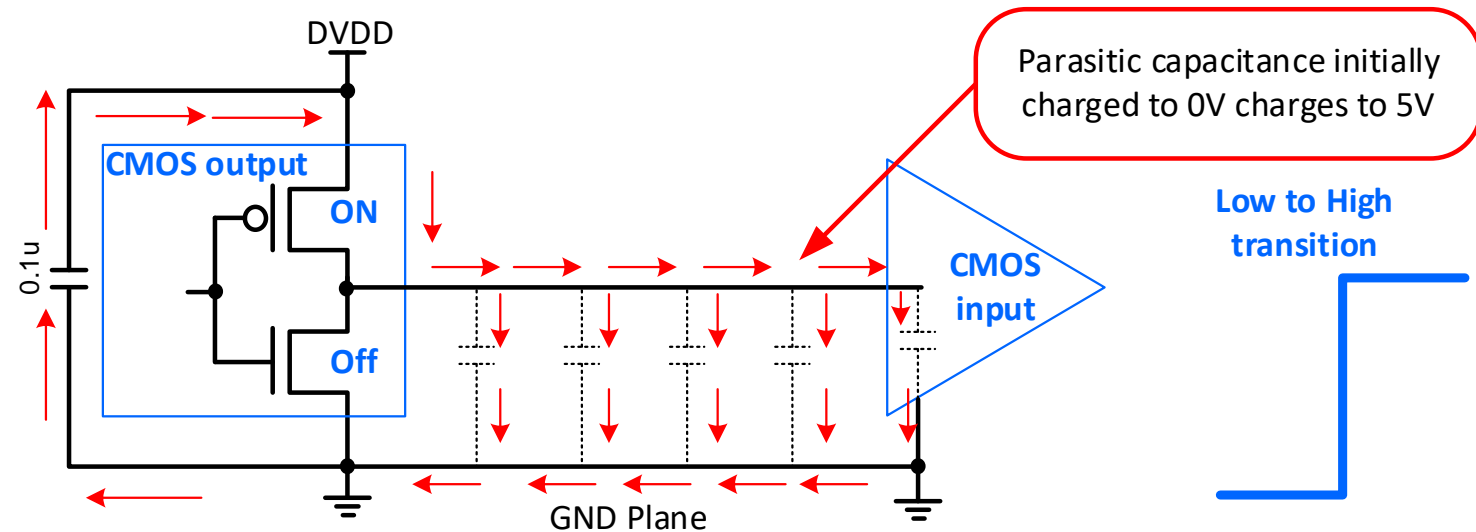Decoupling: How does current flow in GND plane?




Current flow for adjacent GND Plane for microstrip

 - **Low to high transition:** decoupling capacitor supplies transient current to charge parasitic capacitance of bus and CMOS input.
- **High to Low transition:** parasitic capacitance of bus discharge through the CMOS output




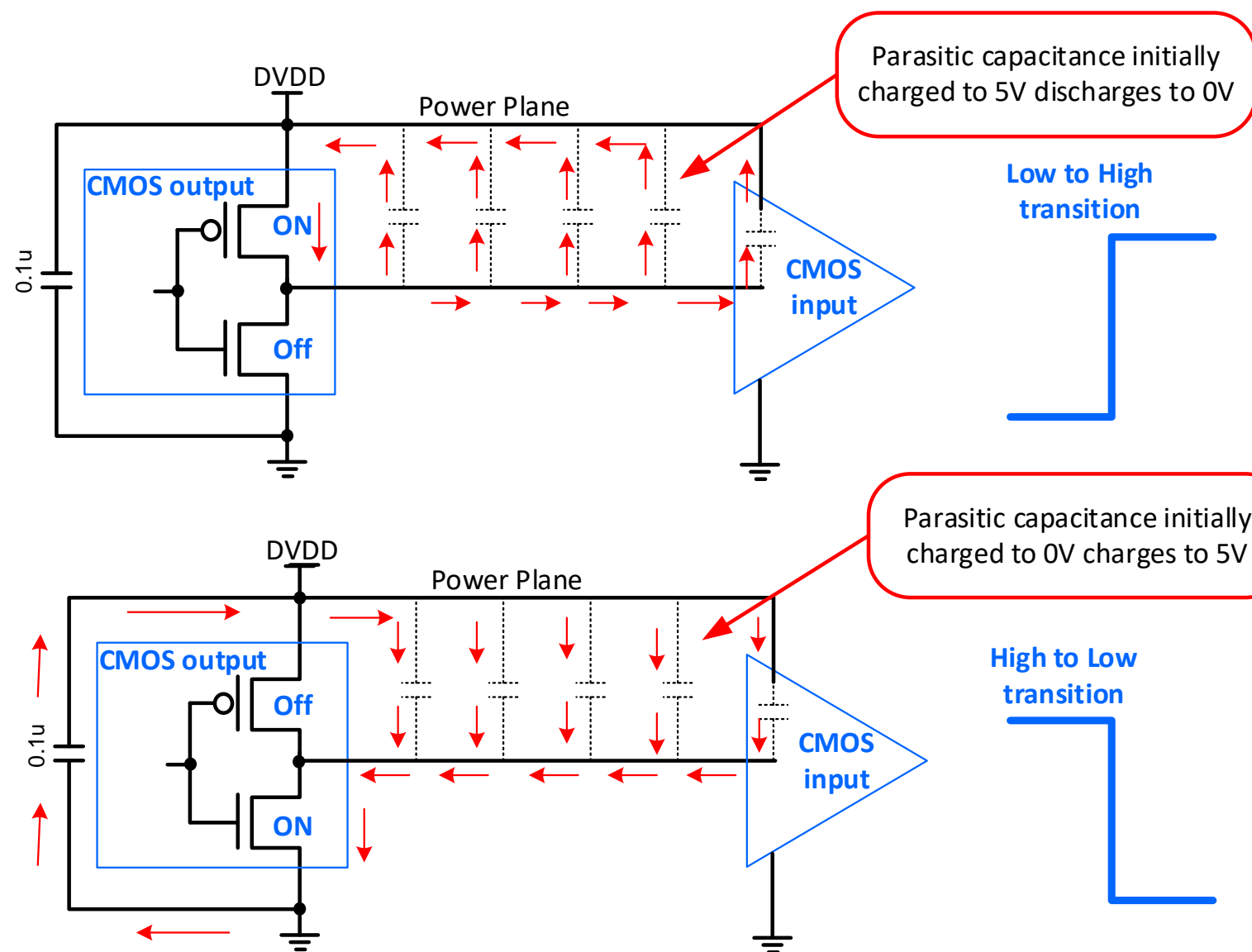Decoupling: How does current flow in power plane?





Current flow for adjacent power Plane for microstrip

 - **Low to high transition:** parasitic capacitance of bus discharge through the CMOS output
- **High to Low transition:** decoupling capacitor supplies transient current to charge parasitic capacitance of bus and CMOS input.



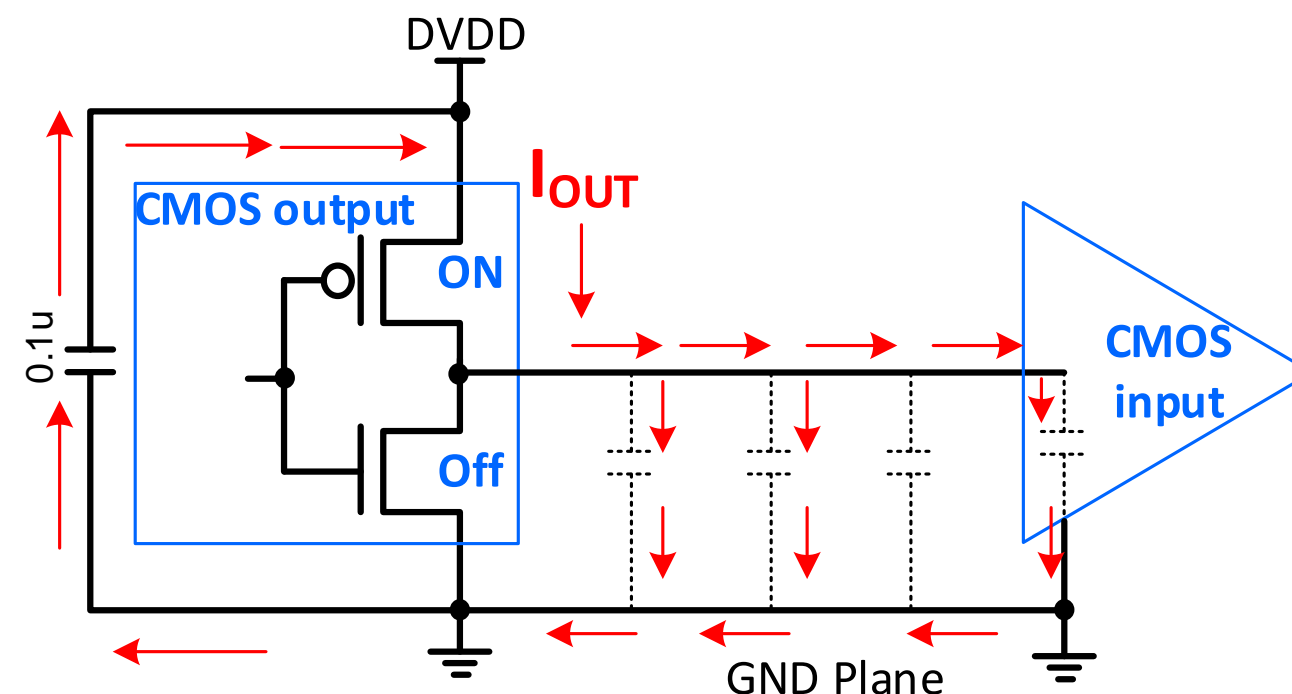 How much current does the decoupling deliver?



Average current during 5ns transition:

$$I_x = \Delta Q / \Delta t = C \cdot \Delta V / \Delta t = 10\text{pF} \cdot 5\text{V} / 5\text{ns} = 10\text{mA}$$

Peak current assuming isosceles triangle

$$I_{pk} = 2I_x = 20\text{mA}$$



Average current in period:

$$I_{avg_per} = \Delta Q / \Delta t = C \cdot \Delta V / \Delta t = 10\text{pF} \cdot 5\text{V} / 20\text{ns} = 3\text{mA}$$

The supply doesn't provide the transient current

DVDD Slowly Recharge
Decoupling between
transients through higher
inductive path

 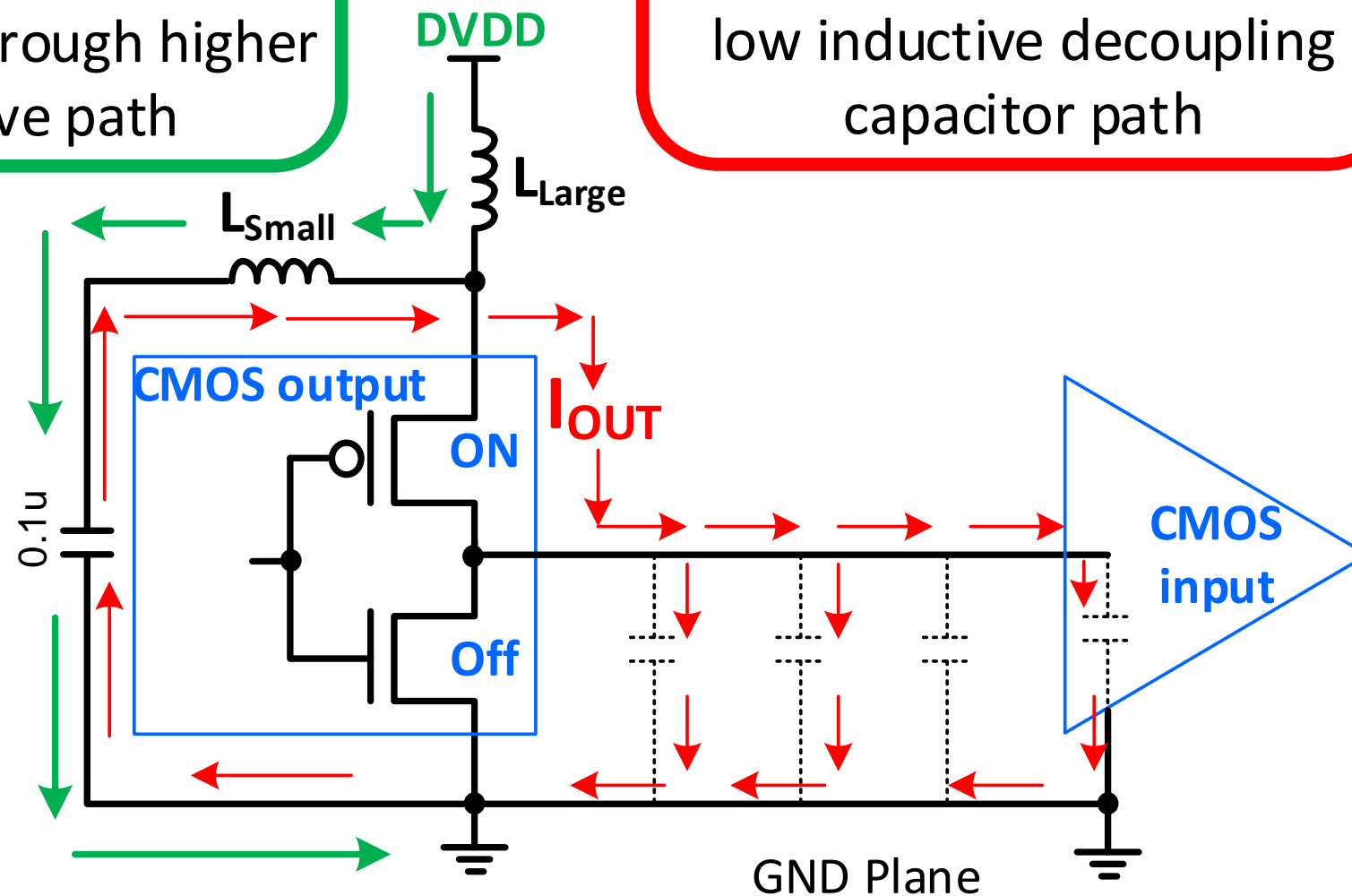I_{out} Digital switching gets
fast transient response from
low inductive decoupling
capacitor path



Thanks for your time!
Please try the quiz.

Quiz: Decoupling capacitors




1. (True/False) Using a large and small value decoupling capacitor is a good way to improve decoupling because the small value decoupling capacitor will be optimal for high frequency. For example, connecting a 0.1uF and a 0.001uF capacitor in parallel is a good combination for better high frequency decoupling.
 - a) True
 - b) False

Quiz: Decoupling capacitors

1. (True/False) Using a large and small value decoupling capacitor is a good way to improve decoupling because the small value decoupling capacitor will be optimal for high frequency. For example, connecting a 0.1 μ F and a 0.001 μ F capacitor in parallel is a good combination for better high frequency decoupling.

a) True

b) False

   


Quiz: Decoupling capacitors

2. (True/False) For low inductance, it is better to place multiple small via than one large one. For example, two 12mil via would have lower inductance than one 20mil via.
 - a) True
 - b) False

3. (True/False) The thickness of the dielectric between the decoupling capacitor and ground plane will impact the decoupling effectiveness.
 - a) True
 - b) False

Quiz: Decoupling capacitors

 4. (True/False) For the layout below, when a signal is being transmitted from the CMOS output to the input, the return current will flow in the ground plane (GND).
- a) True
 - b) False



Thanks for your time!



© Copyright 2022 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.

Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)

