

Aliasing and Anti-aliasing Hands-on Experiment

TIPL 4301-L

TI Precision Labs – ADCs


by Art Kay



Required/Recommended Equipment

- Calculation
 - Simple calculation using Nyquist theorem
 - Verification using Analog Engineer's Calculator
 - Anti-Aliasing filter hand calculations
- Simulation
 - Design of Anti-Aliasing filter using FilterPro™
 - Simulation of Anti-Aliasing filter using OPA320 Model
- Measurement
 - PLABS-SAR-EVM-PDK
 - <http://www.ti.com/tool/plabs-sar-evm-pdk>
 - Download EVM software and purchase EVM


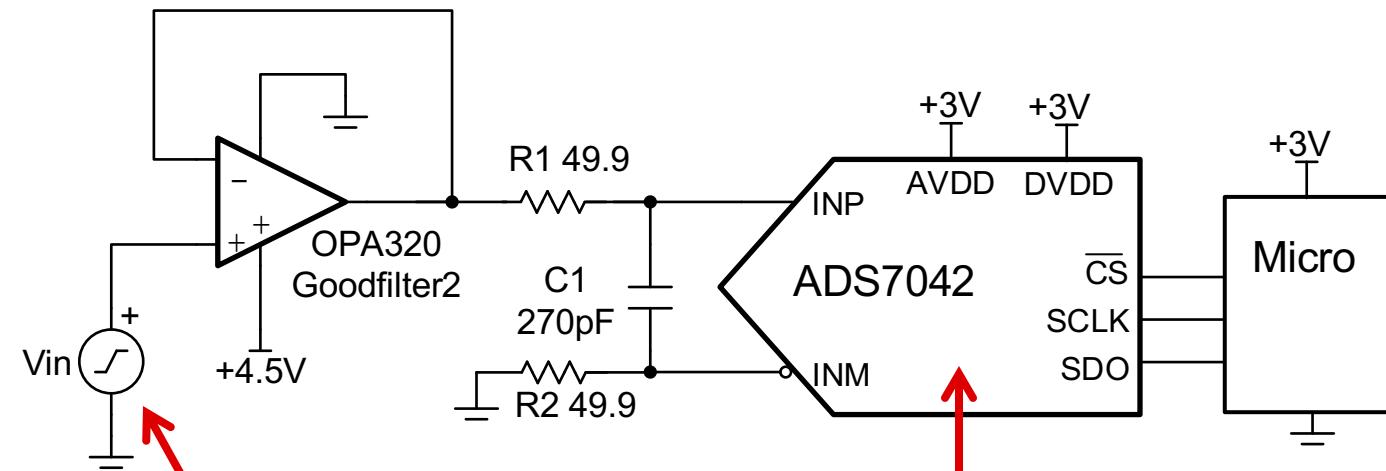
Fill in the Alias frequencies Given f_s and f_{in}




Signal Amplitude:
 $V_{in} = 2.9\text{Vpp}$
 $V_{cm} = 1.5\text{V}$
Normal Operation:
 $f_{in} = 0.1\text{kHz}$
Alias Operation:
 $f_{in} = 10.1\text{kHz}$

Sampling rate:
 $f_s = 10\text{ksps}$



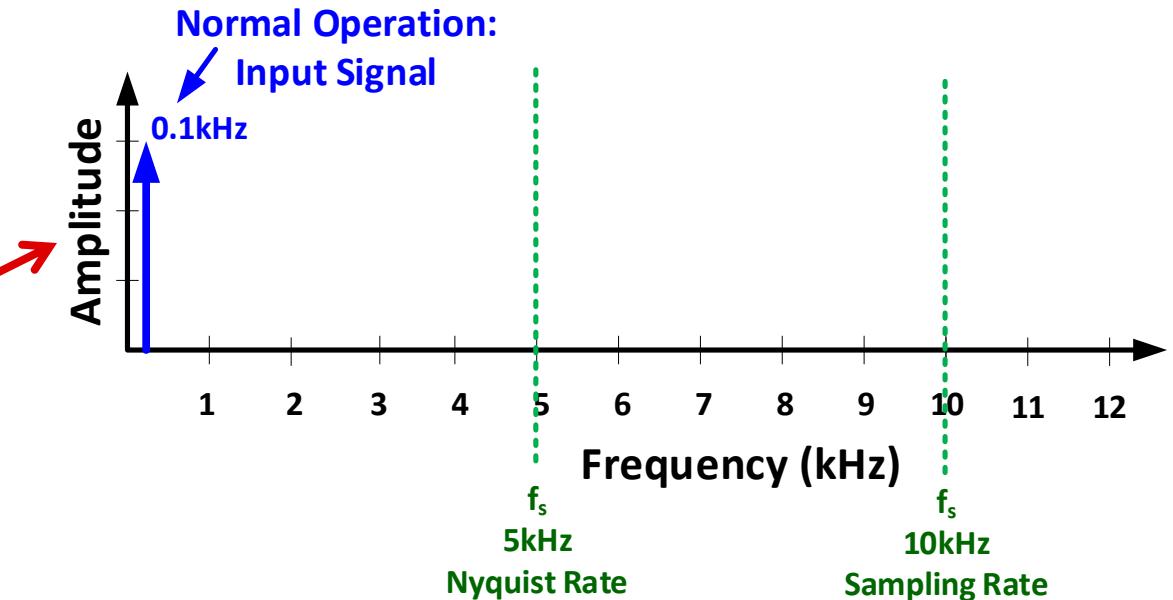
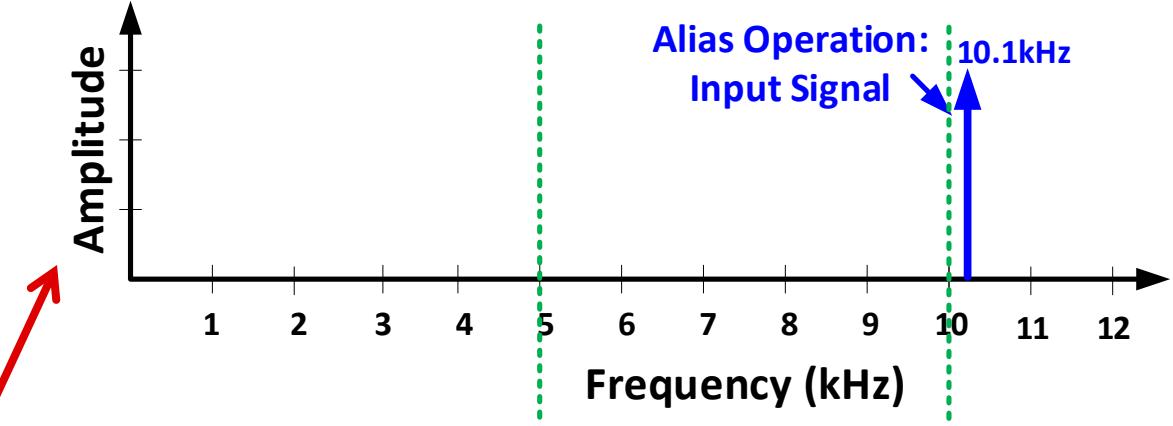
Fill in all the alias frequencies
in the diagrams.



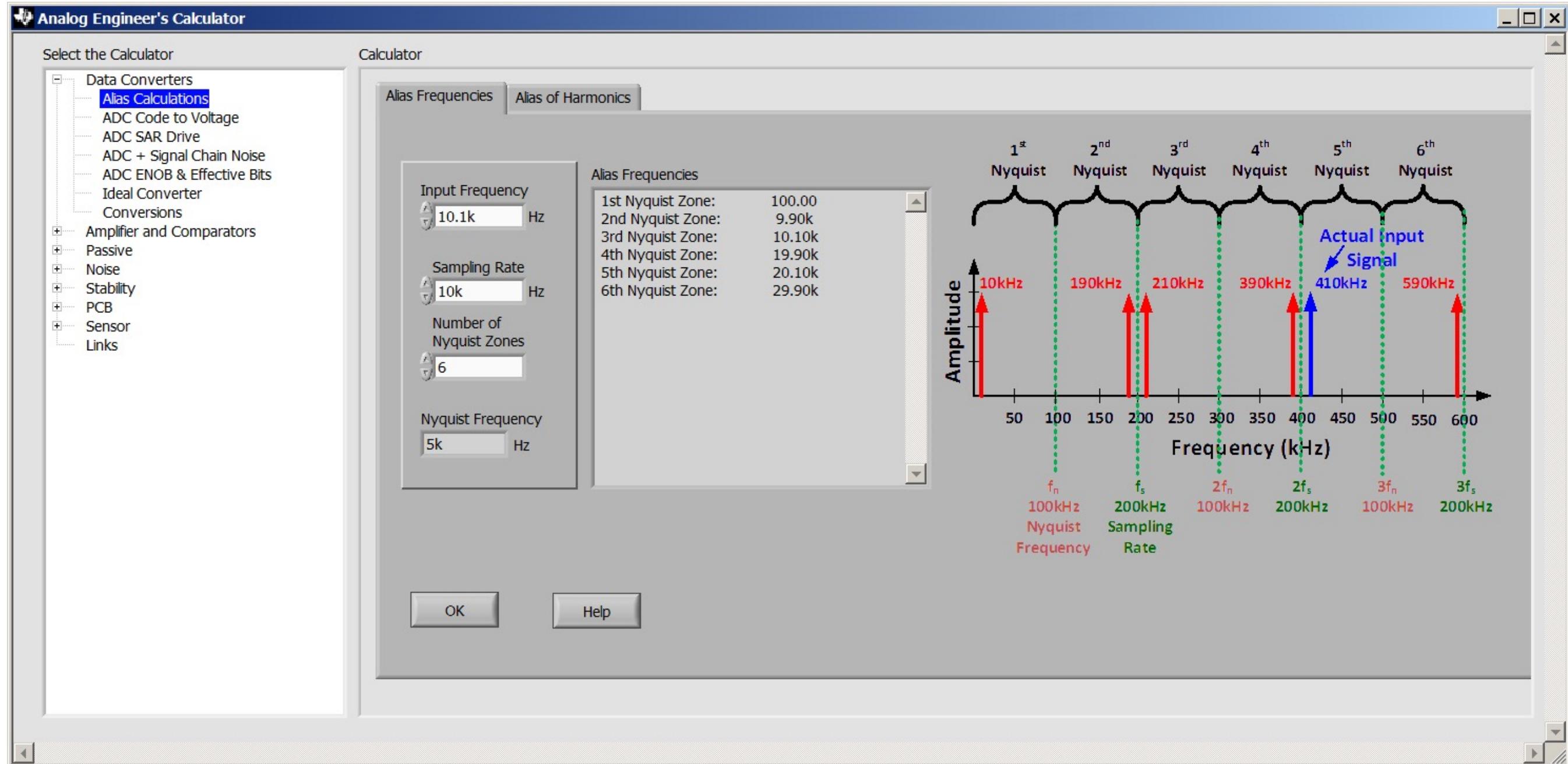Analog Engineers Calculator: find Alias frequencies



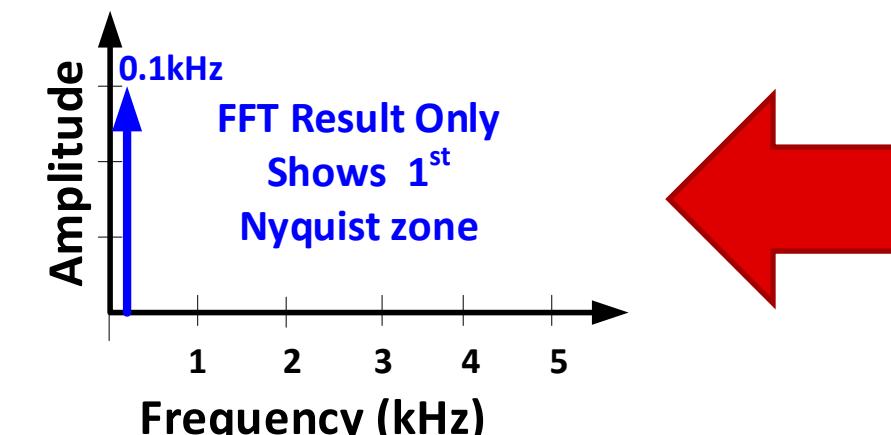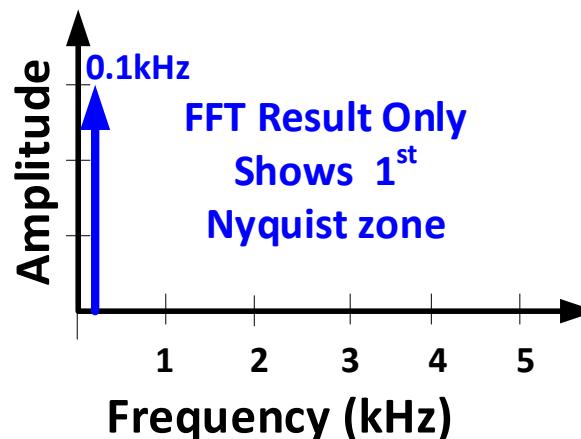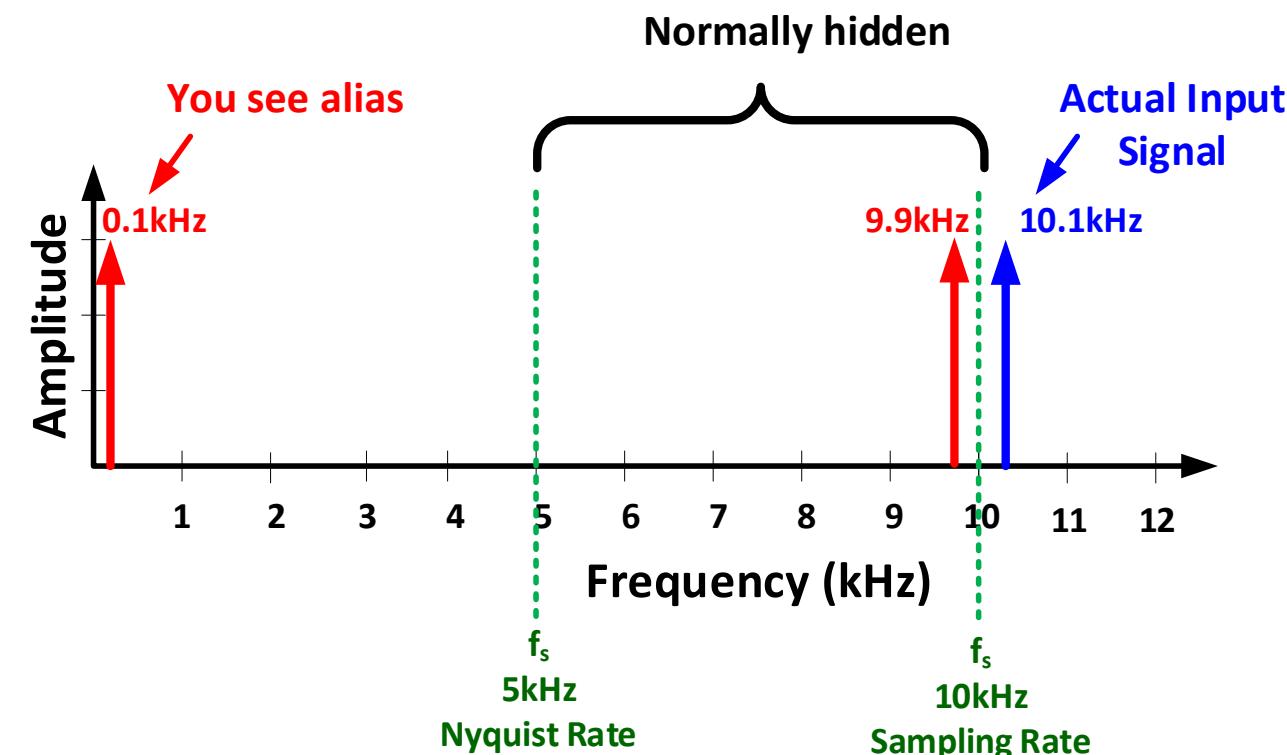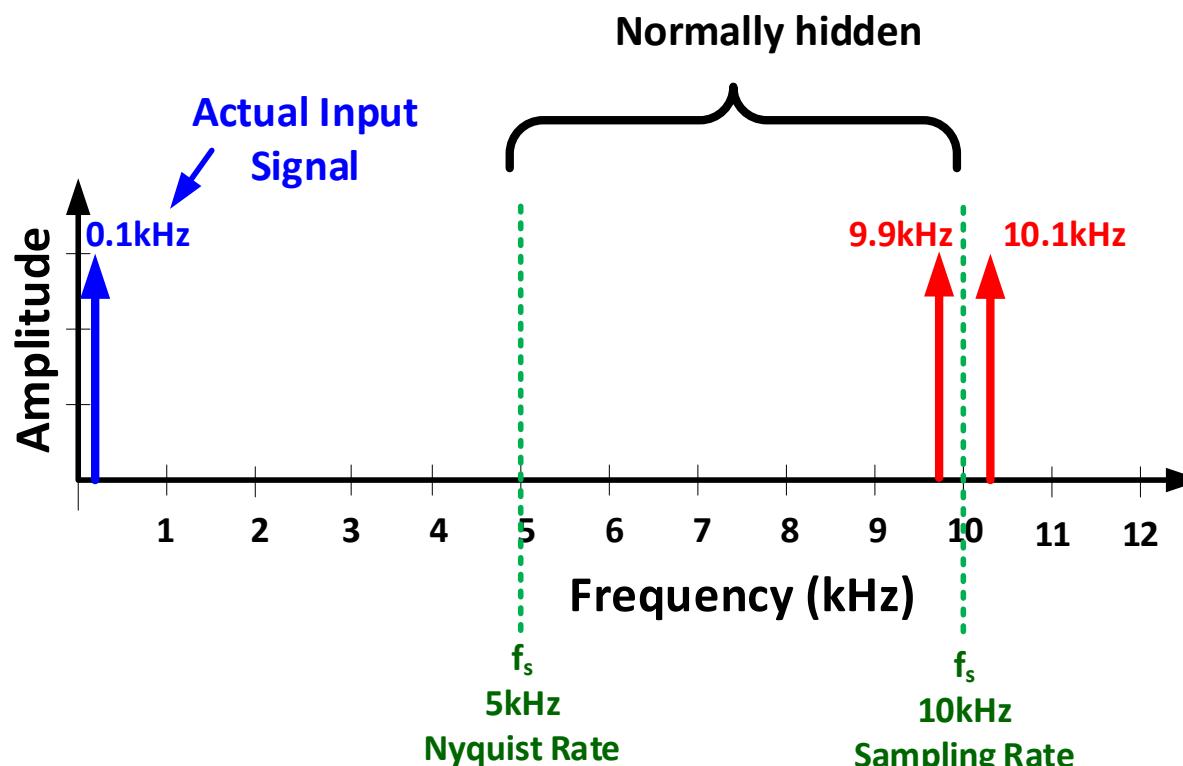Solutions: Normal Operation vs. Aliased Signal



You see the same FFT results for both a 0.1kHz and 10.1kHz input signal.

Hand Calculation to Find Alias Frequencies

Equation

$$f_{alias} = |k \cdot f_s + f_{in}|$$


Where

$k = -N, -2, -1, 0, 1, 2, \dots, N$

N = Nyquist Zones

f_s = sampling rate

f_{in} = input frequency

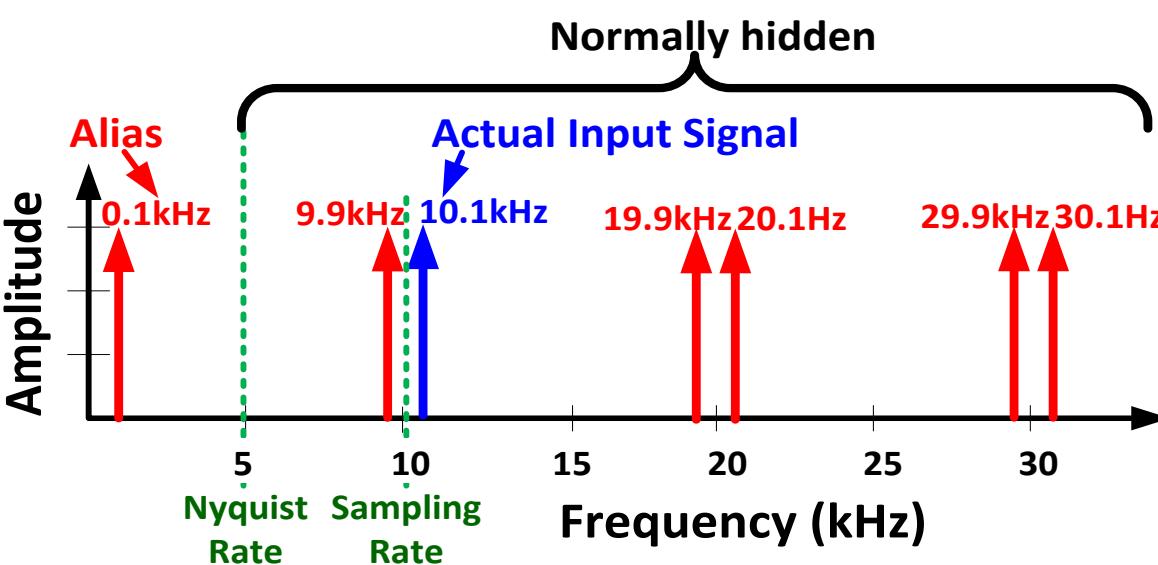

Example

$$k = \dots, -4, -3, -2, -1, 0, 1, 2, \dots$$

$$f_s = 10\text{kHz}$$

$$f_{in} = 10.1\text{kHz}$$

$$f_{alias} = |n \cdot f_s + f_{in}|$$

$$f_{alias}(-4) = |-4 \cdot 10\text{kHz} + 10.1\text{kHz}| = 29.9\text{kHz}$$

$$f_{alias}(-3) = |-3 \cdot 10\text{kHz} + 10.1\text{kHz}| = 19.9\text{kHz}$$

$$f_{alias}(-2) = |-2 \cdot 10\text{kHz} + 10.1\text{kHz}| = 9.9\text{kHz}$$

$$f_{alias}(-1) = |-1 \cdot 10\text{kHz} + 10.1\text{kHz}| = 0.1\text{kHz}$$

$$f_{alias}(0) = (0 \cdot 10\text{kHz} + 10.1\text{kHz}) = 10.1\text{kHz}$$

$$f_{alias}(1) = (1 \cdot 10\text{kHz} + 10.1\text{kHz}) = 20.1\text{kHz}$$

$$f_{alias}(2) = (2 \cdot 10\text{kHz} + 10.1\text{kHz}) = 30.1\text{kHz}$$

Design an Anti-aliasing Filter: find Cutoff

System Requirements

$f_s = 10\text{kHz}$, $f_{\text{Nyquist}} = 5\text{kHz}$

$V_{\text{in@Nyquist}} = 20\text{mVpp}$, FSR = 3V


Resolution = 12 bits

Filter Specifications:

2nd Order Filter, find f_c

Goal:

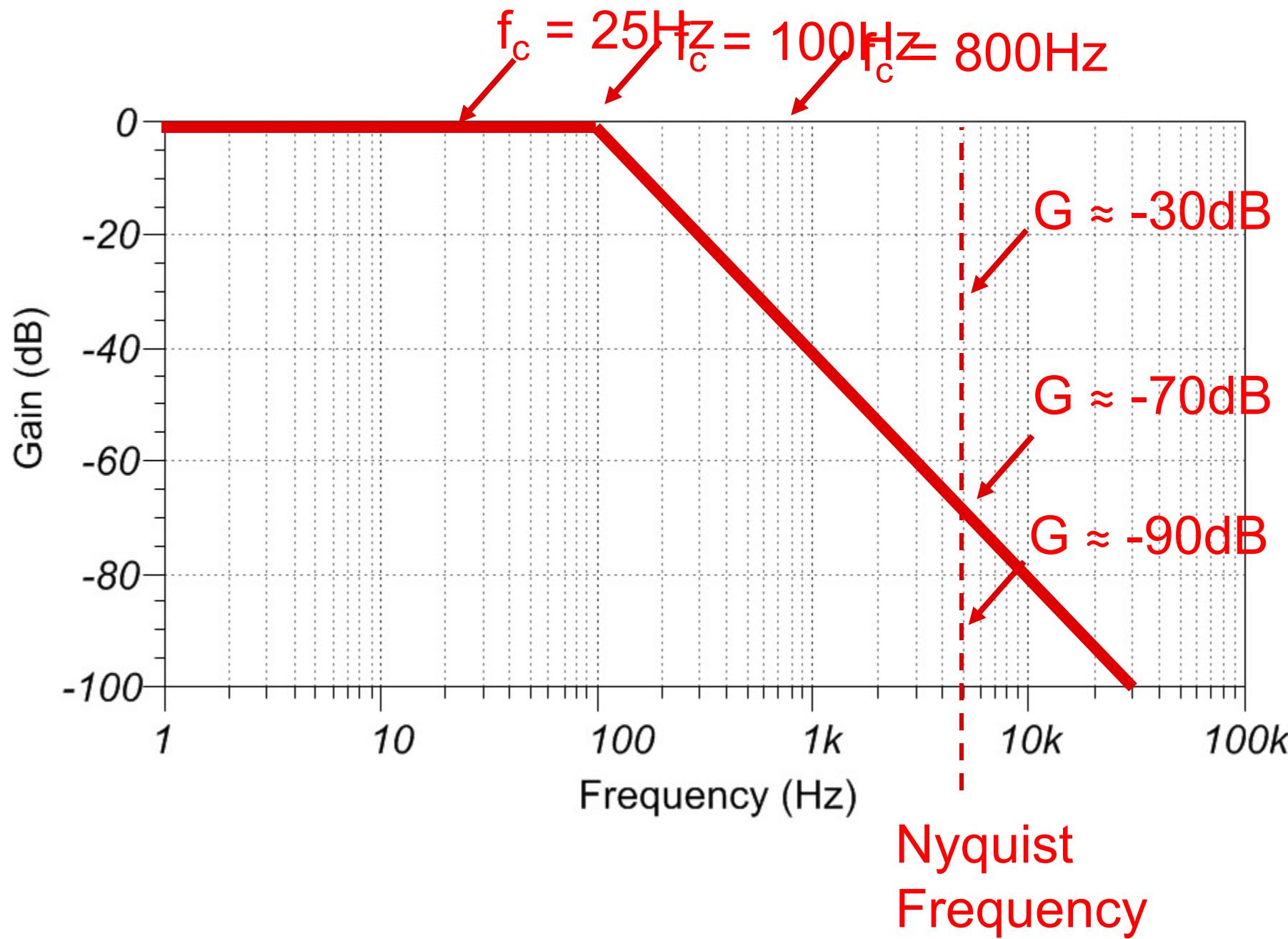Find f_c to attenuate the 20mVpp alias at the Nyquist frequency to less than half an LSB.



Design an Anti-aliasing Filter: find Cutoff

System Requirements

$f_s = 10\text{kHz}$, $f_{\text{Nyquist}} = 5\text{kHz}$
 $V_{\text{in@Nyquist}} = 20\text{mVpp}$, $\text{FSR} = 3\text{V}$

Resolution = 12 bits

Filter Specifications:

2nd Order Filter, find f_c

Goal:

Find f_c to attenuate the 20mV alias at the Nyquist frequency to less than half an LSB.

$$0.5\text{LSB} = 0.5 \left(\frac{\text{FSR}}{2^N} \right) = 0.5 \left(\frac{3\text{V}}{2^{12}} \right) = 366\mu\text{V}$$

Find the required attenuation


$$G = \frac{0.5\text{LSB}}{V_{\text{in@Nyquist}}} = \frac{366\mu\text{V}}{20\text{mV}} = 18.31\text{mV/V}, -34.7\text{dB}$$

Find f_c for $G = 18.31\text{mV/V}$ at $f = f_{\text{Nyquist}} = 5\text{kHz}$

$$|G(f)| = \frac{1.622}{\sqrt{\left(\frac{f}{f_c}\right)^4 + 1.622\left(\frac{f}{f_c}\right)^2 + 2.631}}$$

Not a closed form equation!

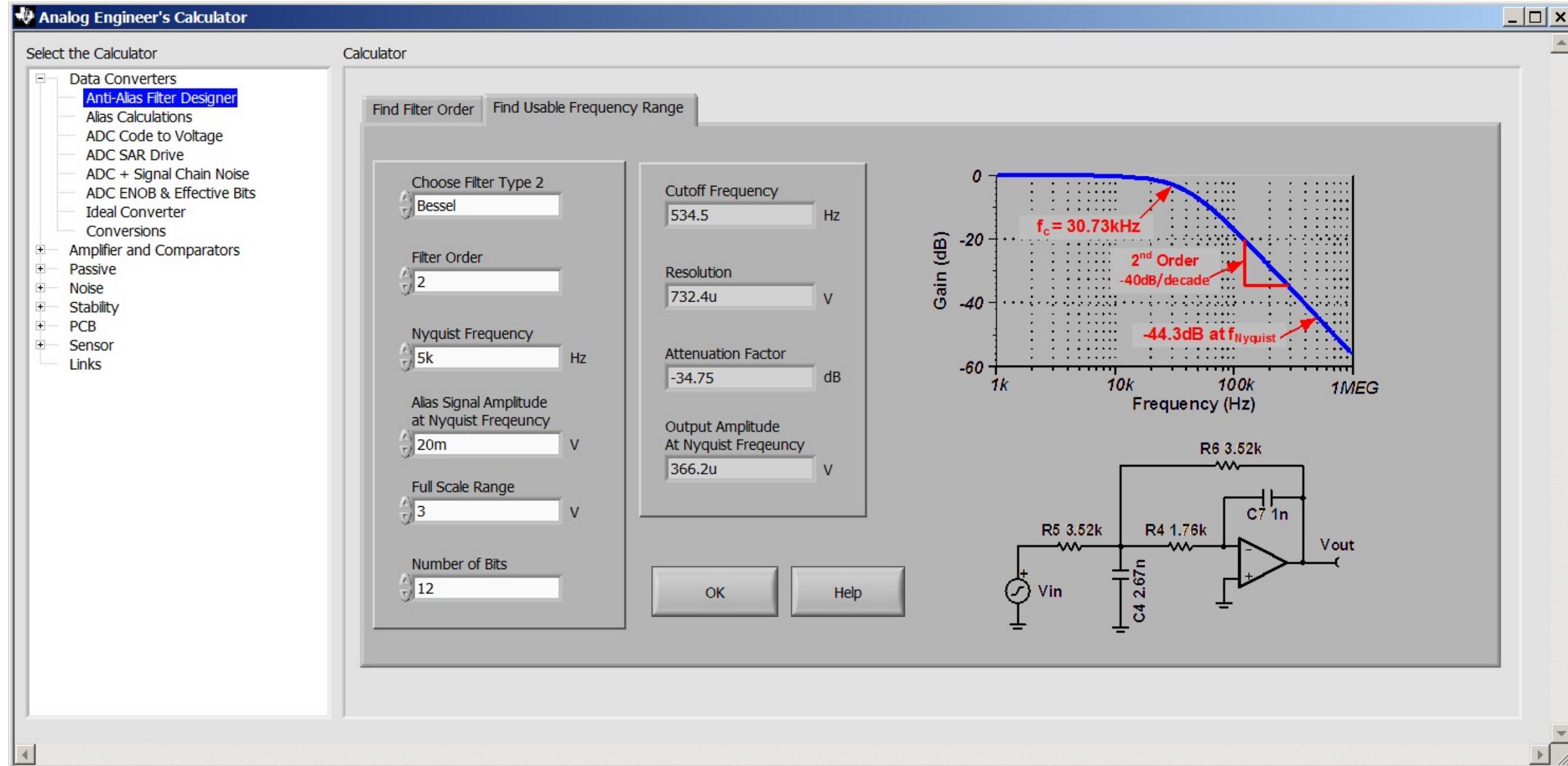Calculator: Find Antialiasing Filter Cutoff



Design an Anti-aliasing Filter: find Order

System Requirements

$f_s = 10\text{kHz}$, $f_{\text{Nyquist}} = 5\text{kHz}$

$V_{\text{in@Nyquist}} = 20\text{mV}$, FSR = 3V


Resolution = 12 bits

Filter Specifications:


$f_c = 1\text{kHz}$, find Order

Goal:

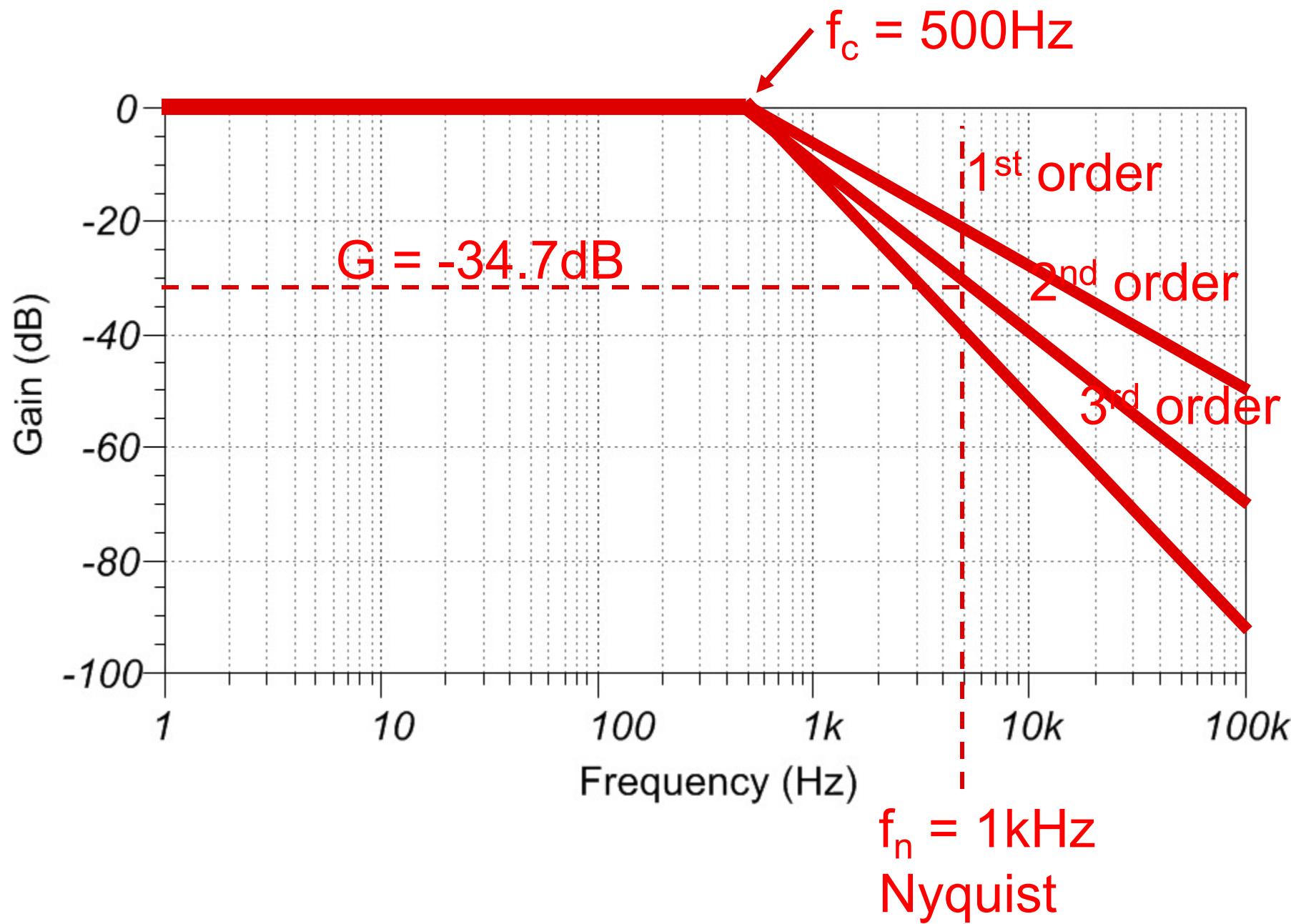Find the order to attenuate the 20mV alias at the Nyquist frequency to less than half an LSB. From previous design Gain is -34.7dB.



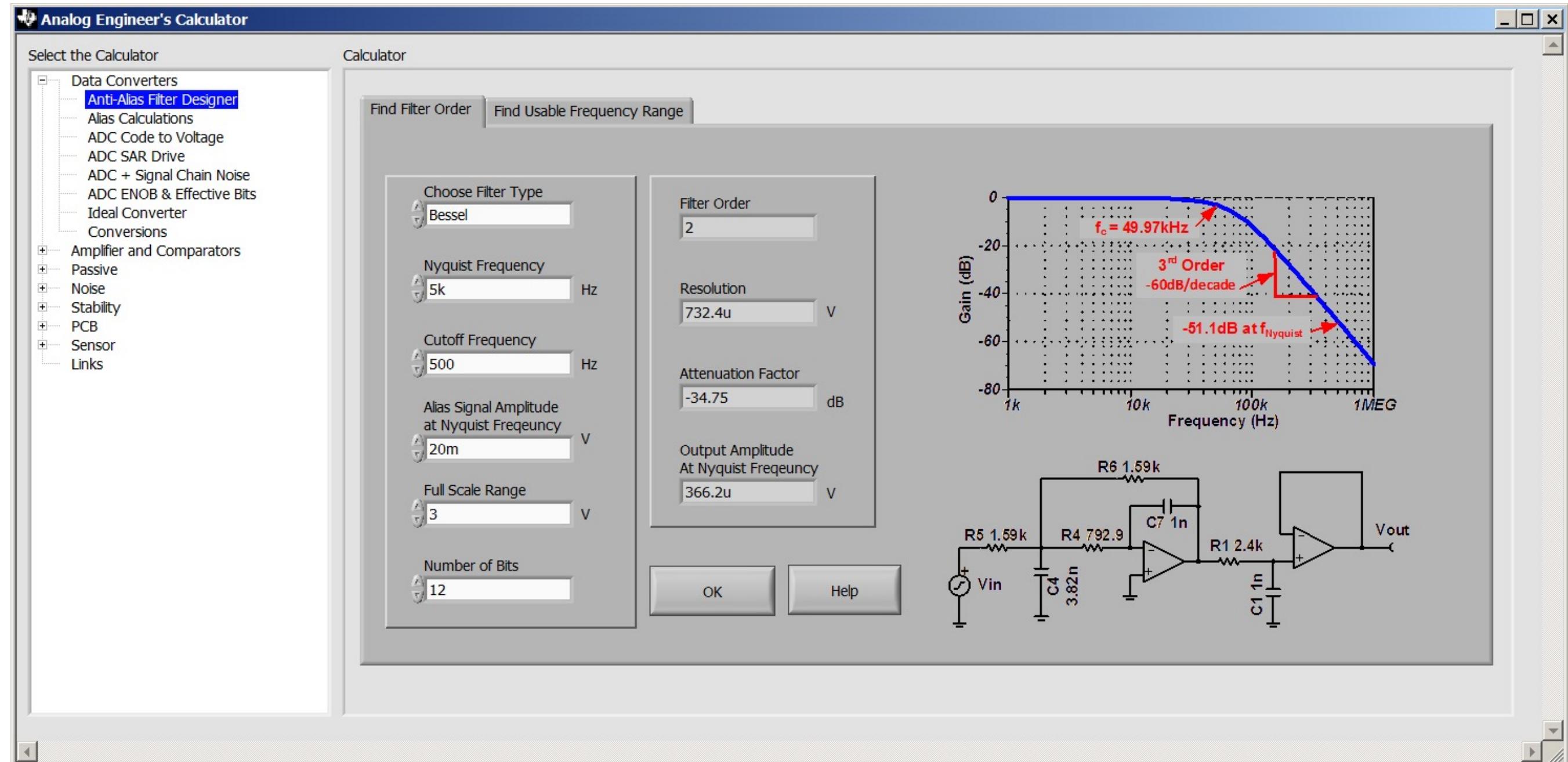Calculator: Find Antialiasing Filter Order




Designing the Antialiasing filter

- Download FilterPro v3.1
- <http://www.ti.com/filterpro-dt>
- Active filter design software.


Run from
Texas Instruments > FilterPro Desktop



Designing the Antialiasing filter

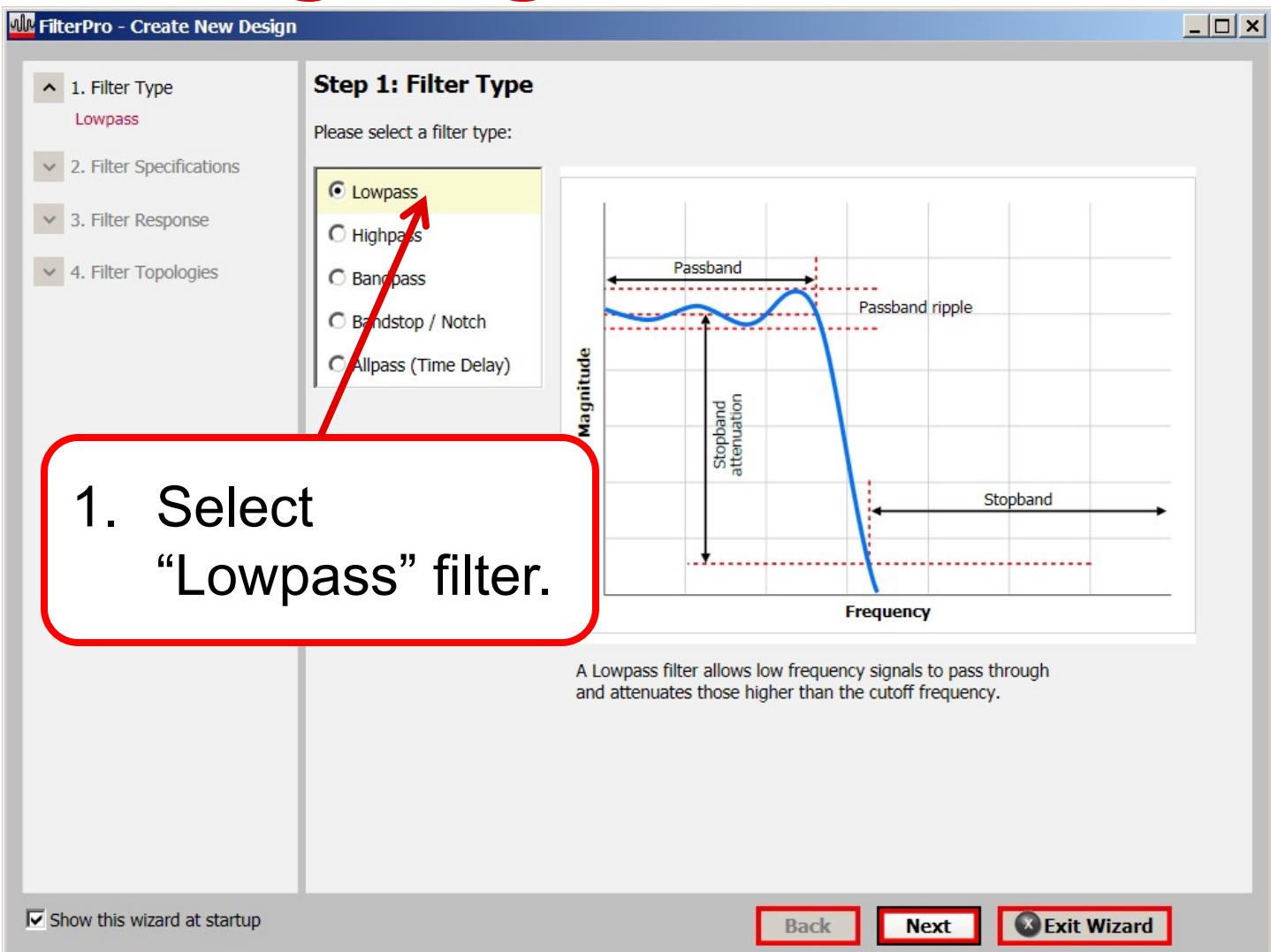


1. Select
“Lowpass” filter.

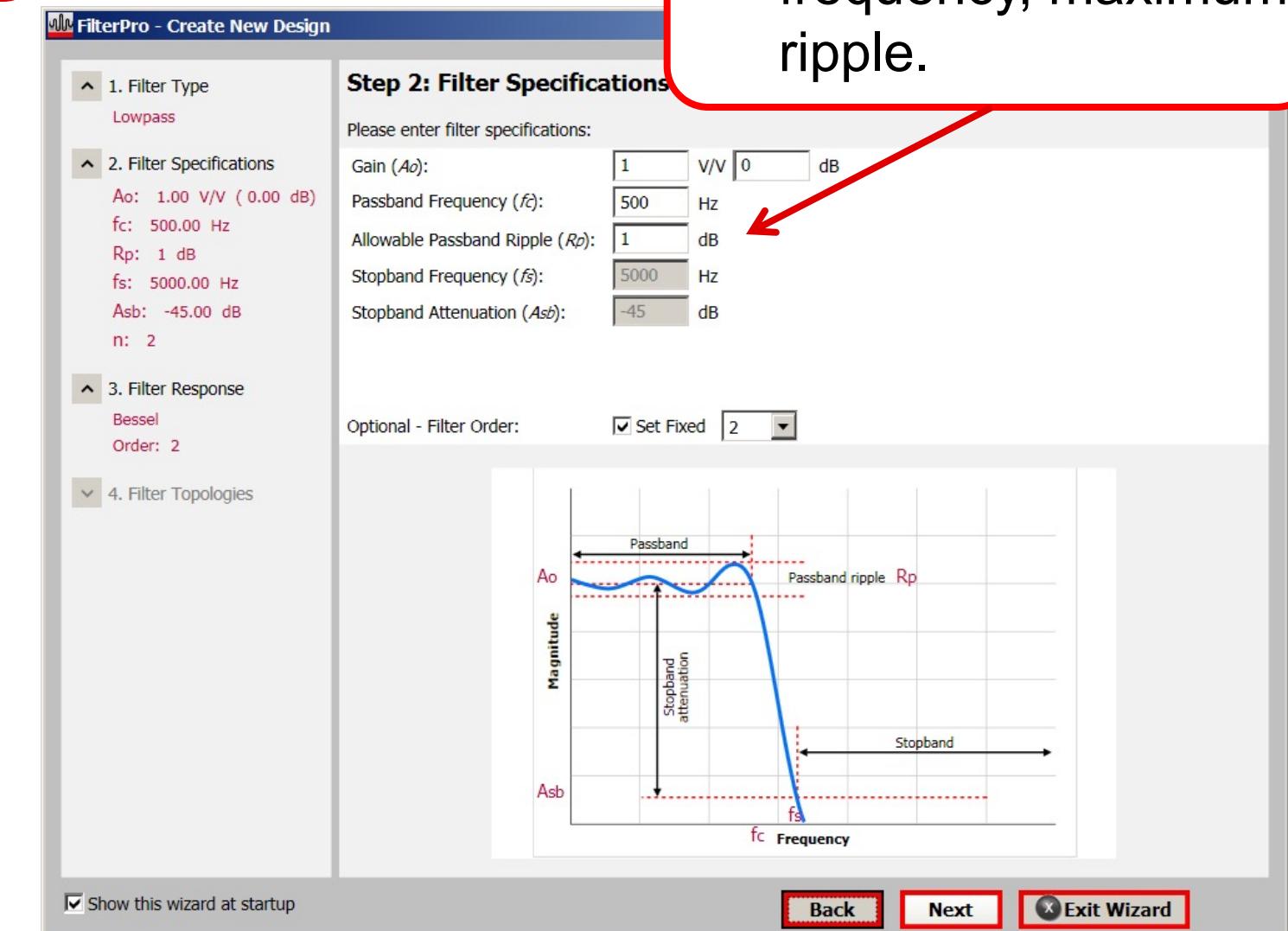


2. Enter gain, cutoff frequency, maximum ripple.

Designing the Antialiasing filter

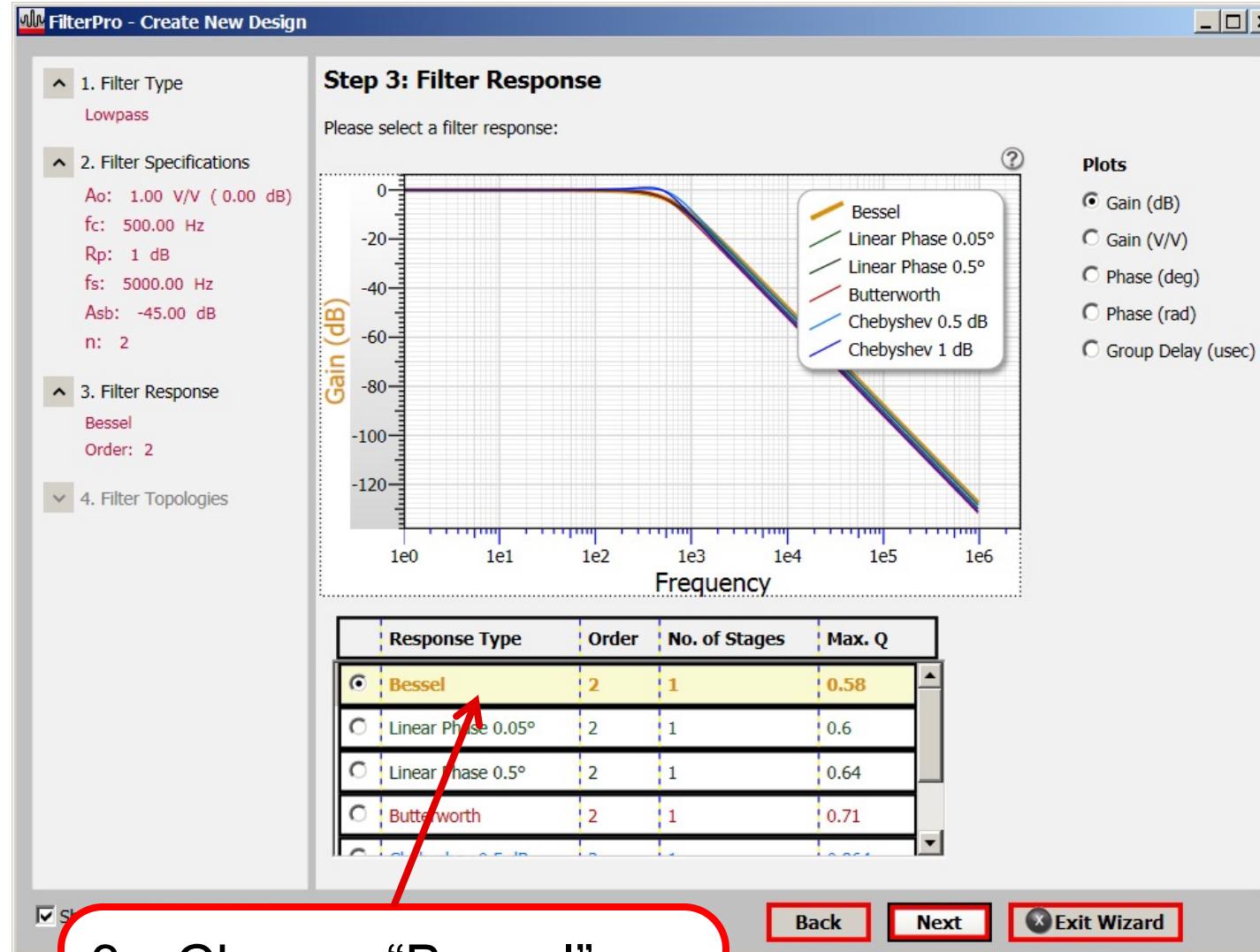

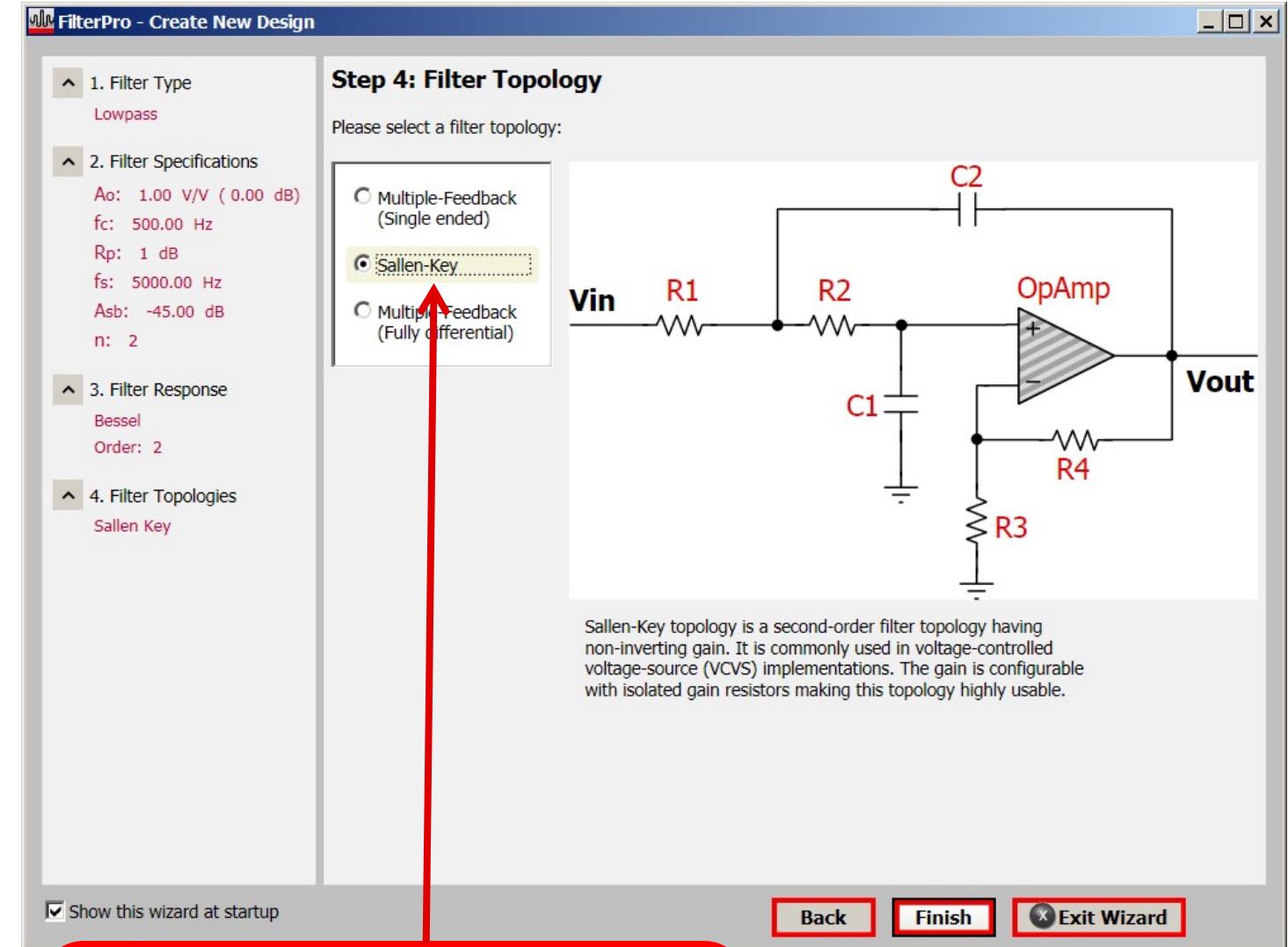3. Choose “Bessel” type for maximally flat response.



4. Choose “Sallen-Key” topology for non-inverting functionality.

Designing the Antialiasing filter

5. The default tolerance is “exact”. Change according to your design.

6. Click on the component value “150nF” and change to “10nF”.

Filter Pro Desktop - Untitled *

Name: Lowpass, Sallen Key, Bessel Part: Ideal Opamp Order: 2 Number Of Stages: 1

Gain: 1 V/V (0 dB) Allowable PassBand Ripple: 1 dB Passband Frequency: 500 Hz Corner Frequency Attenuation: -3 dB

Reset Component Tolerances - Resistors Exact: 0% Capacitors Exact: 0%

DesignTree

OpAmp

R1 2.16KΩ R2 2.16KΩ C2 133.35nF C1 100nF

Filter Stage: 1 Passband Gain(Ao): 1 Cutoff Frequency(f_n): 637 Hz

Actual Gain (dB) Actual Phase (deg)

Actual Group Delay (uSec) Phase (deg)

Group Delay (uSec) Frequency (Hz)

v: 3.1.0.23446 Texas Instruments

Filter Pro Desktop - Untitled *

Name: Lowpass, Sallen Key, Bessel Part: Ideal Opamp Order: 2 Number Of Stages: 1

Gain: 1 V/V (0 dB) Allowable PassBand Ripple: 1 dB Passband Frequency: 500 Hz Corner Frequency Attenuation: -3 dB

Reset Component Tolerances - Resistors E96: 1% Capacitors E24: 5%

OpAmp

R1 1.43KΩ R2 2.87KΩ C2 150nF C1 100nF

Filter Stage: 1 Passband Gain(Ao): 1 Cutoff Frequency(f_n): 637 Hz

Actual Gain (dB) Original Gain (dB)


Actual Phase (deg) Original Phase (deg)

Actual Group Delay (uSec) Original Group Delay (uSec)



Group Delay (uSec) Frequency (Hz)

v: 3.1.0.23446 Texas Instruments

Designing the Antialiasing filter

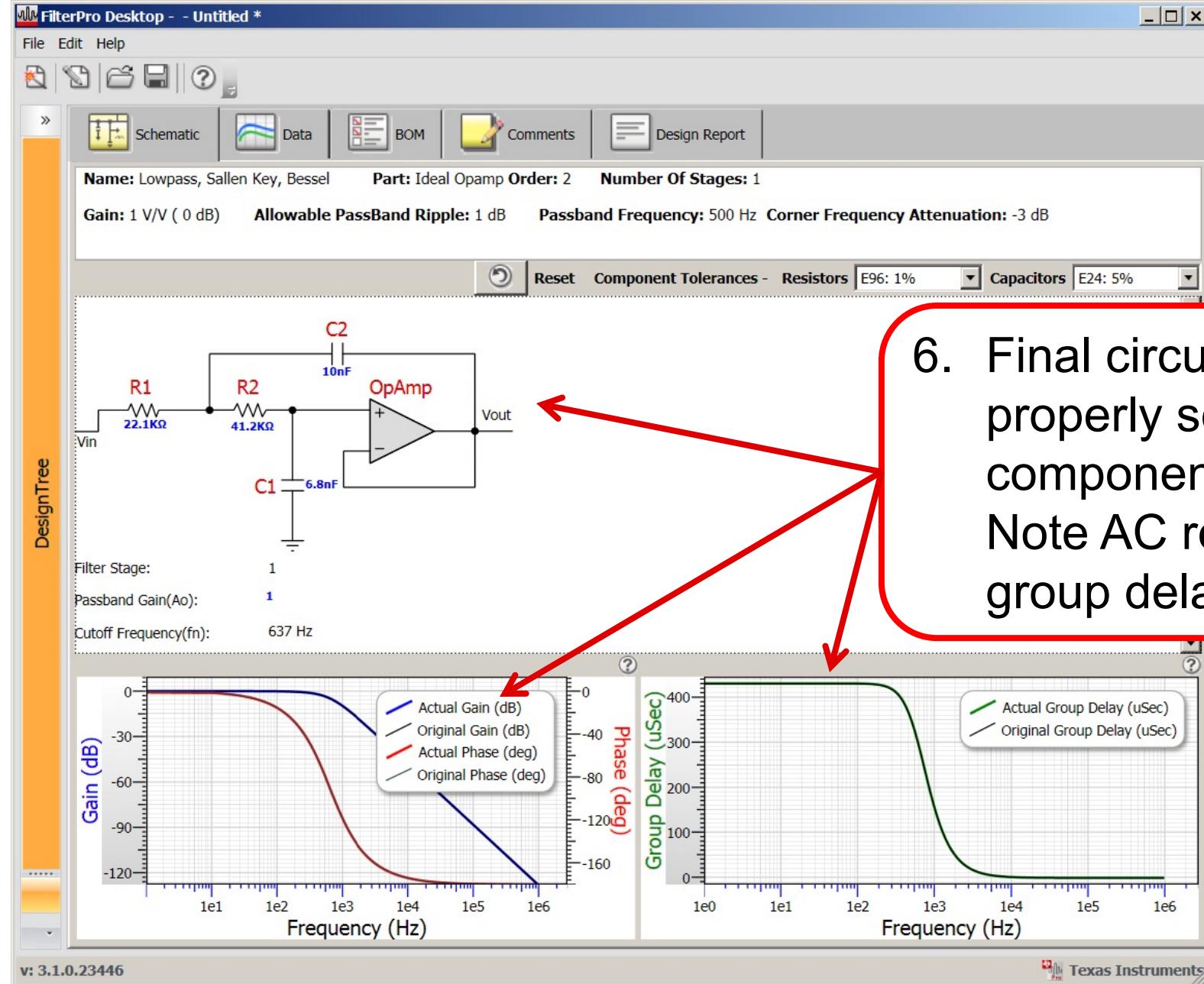

Add an Antialiasing Sallen-Key Filter

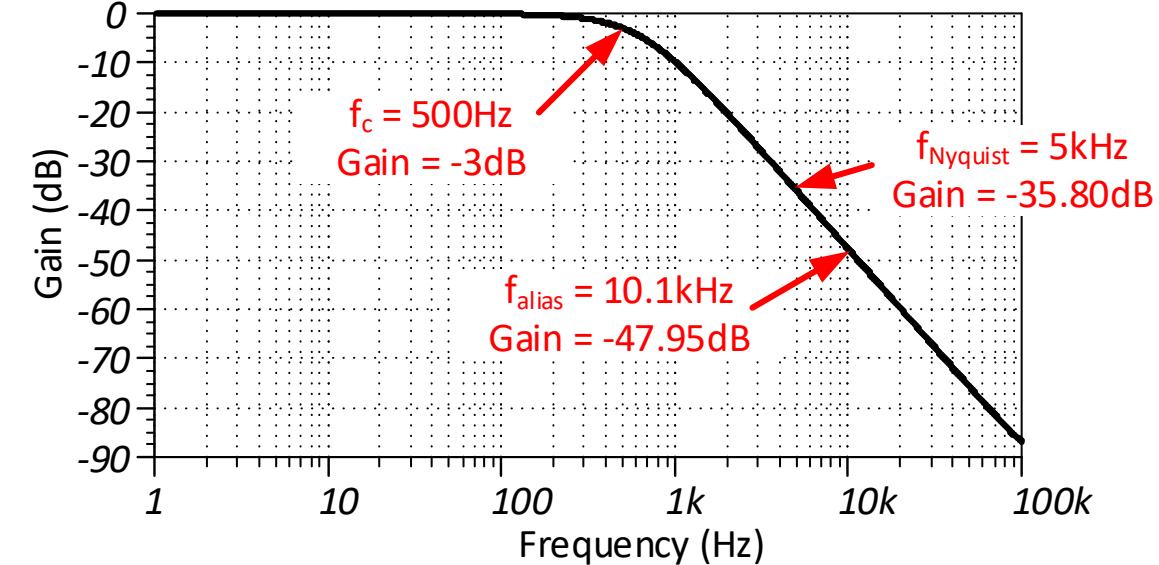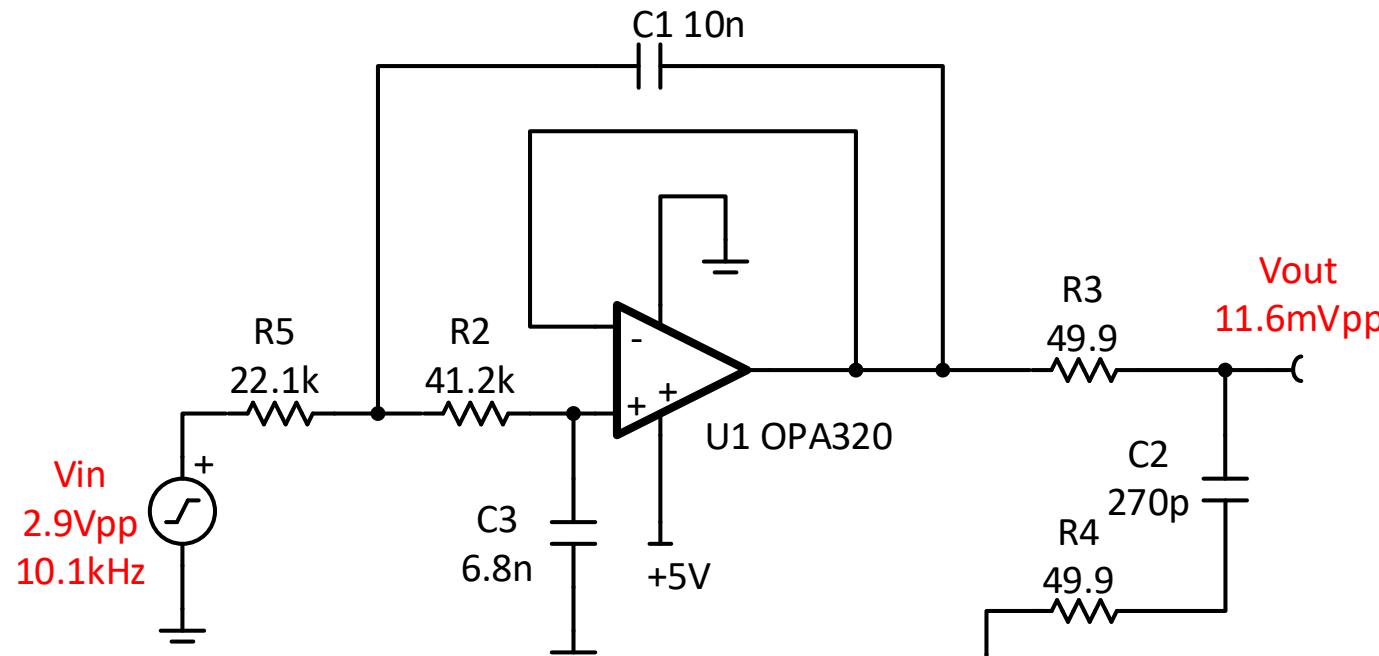


Output at 10.1kHz

$$V_{out} = (2.9V) \cdot \left(10^{\left(\frac{-47.95dB}{20} \right)} \right) = 11.6mV$$

**V_{in}
10.1kHz, 2.9Vpp**

**V_{out}
10.1kHz, 11.6mVpp**




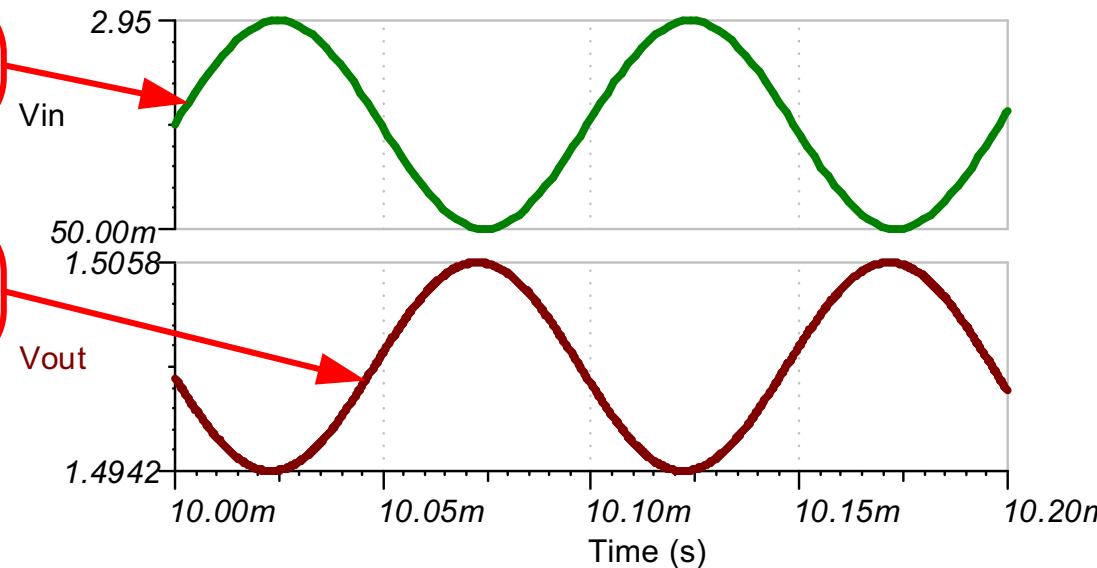


Click here to open TINA file.




OPA320_SK-Filter.TSC


OPA320_Goodfilter2 vs. Sallen-Key Filter

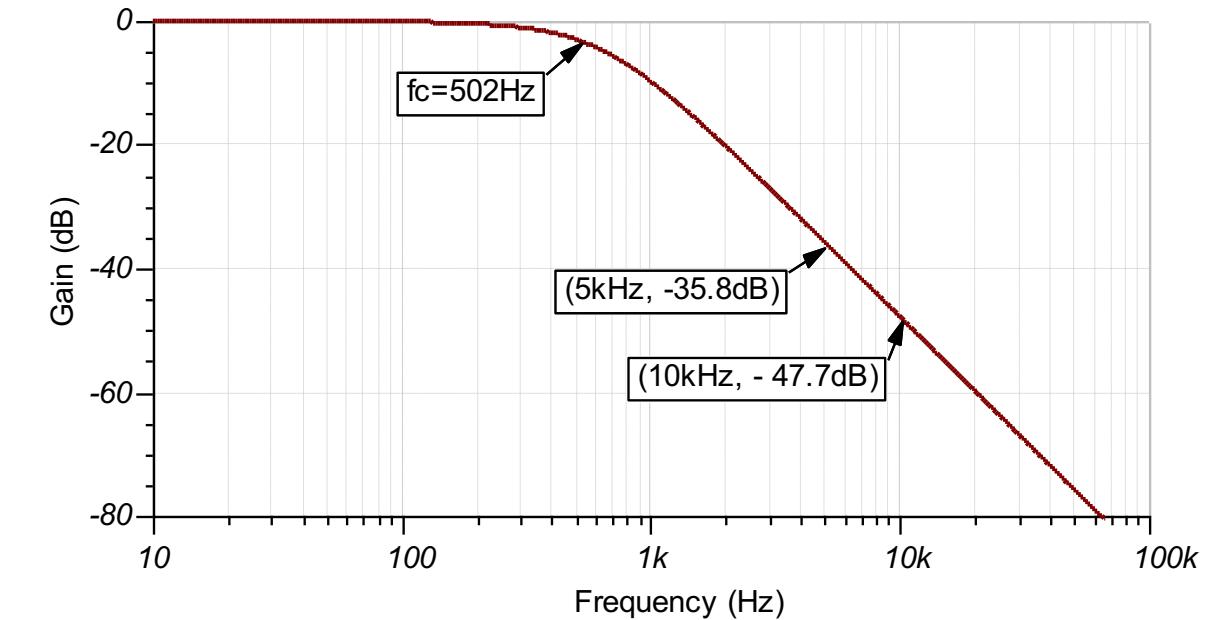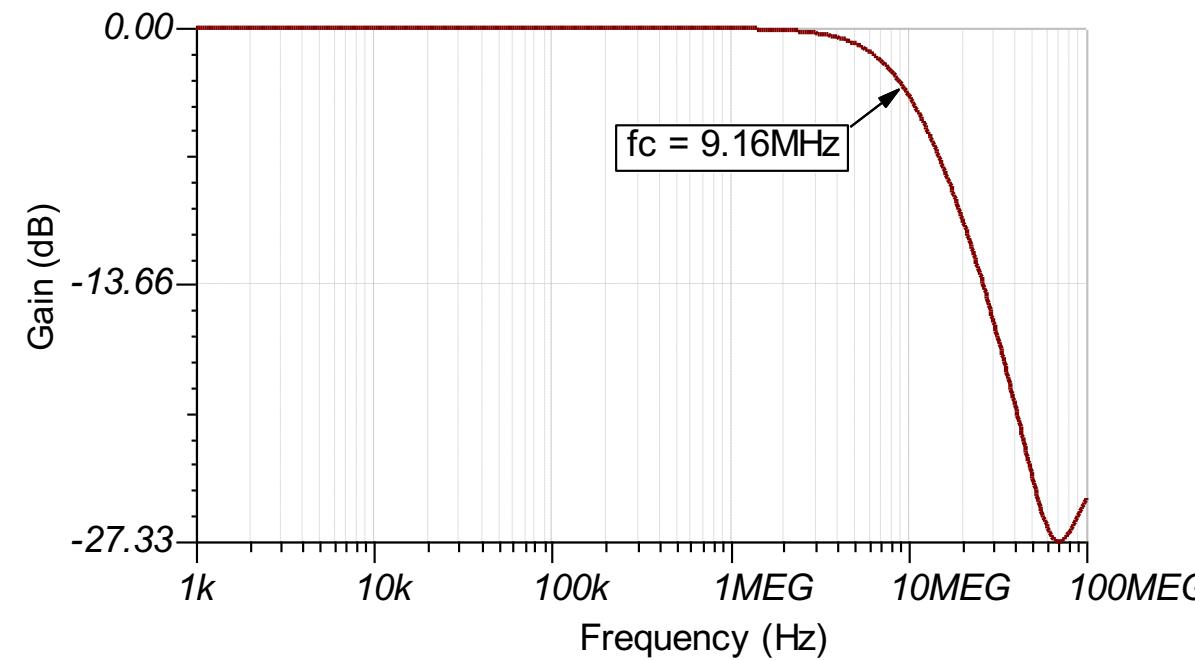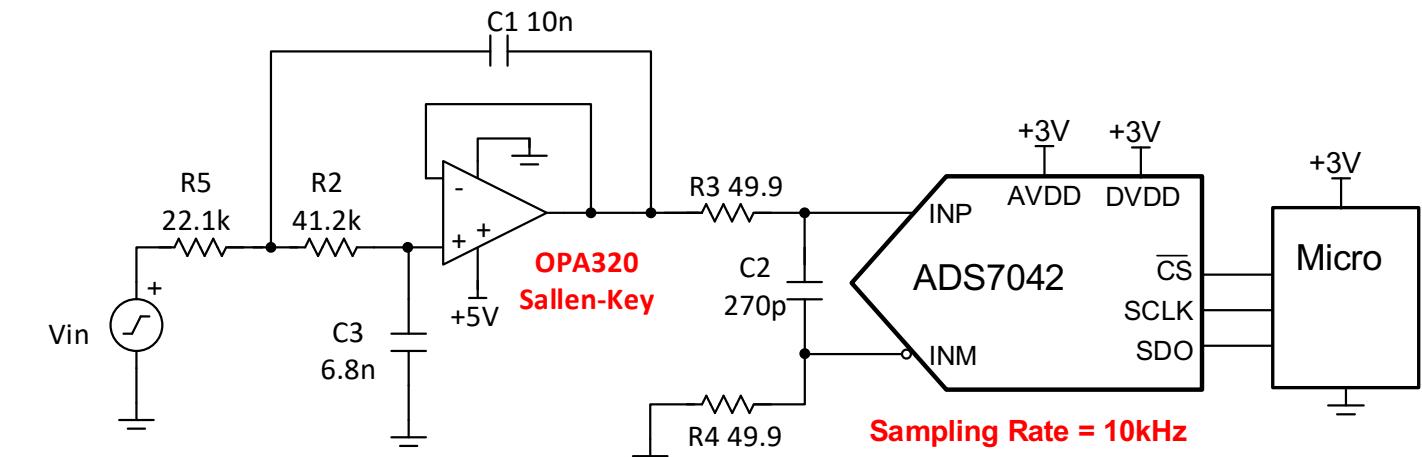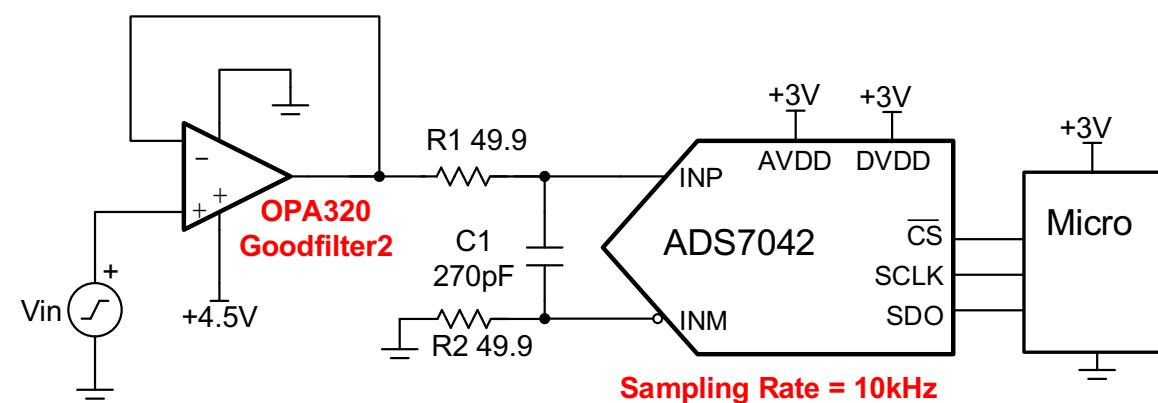

Connect the hardware

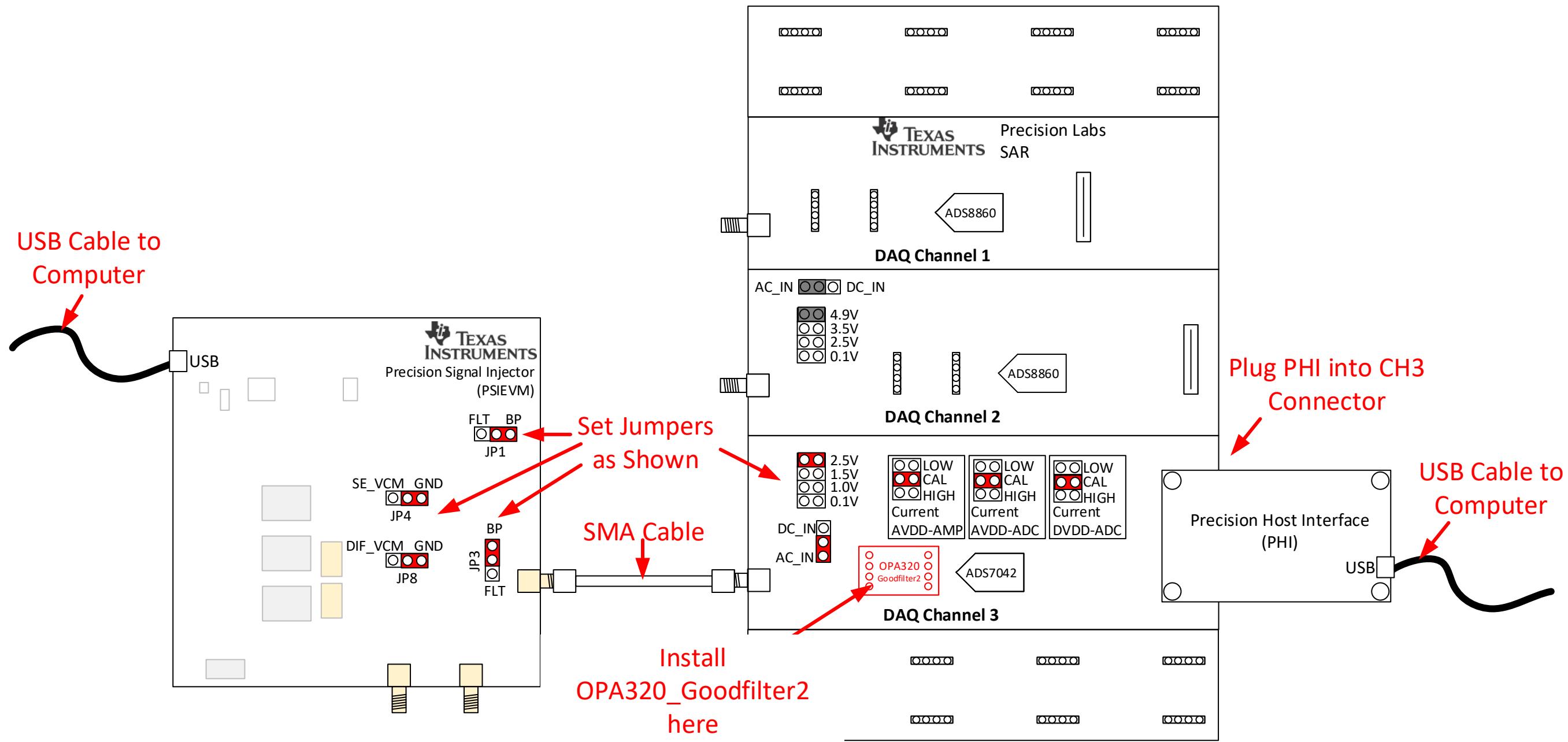


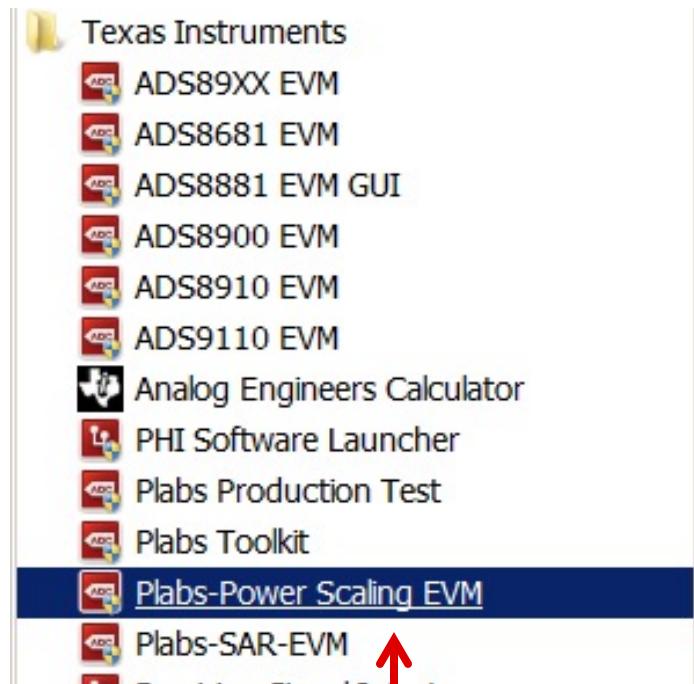Start & Setup the Plabs-Power Scaling EVM Software




1. Select “Plabs-Power Scaling” from “start>All Programs”

2. Set number of samples to 16,384.

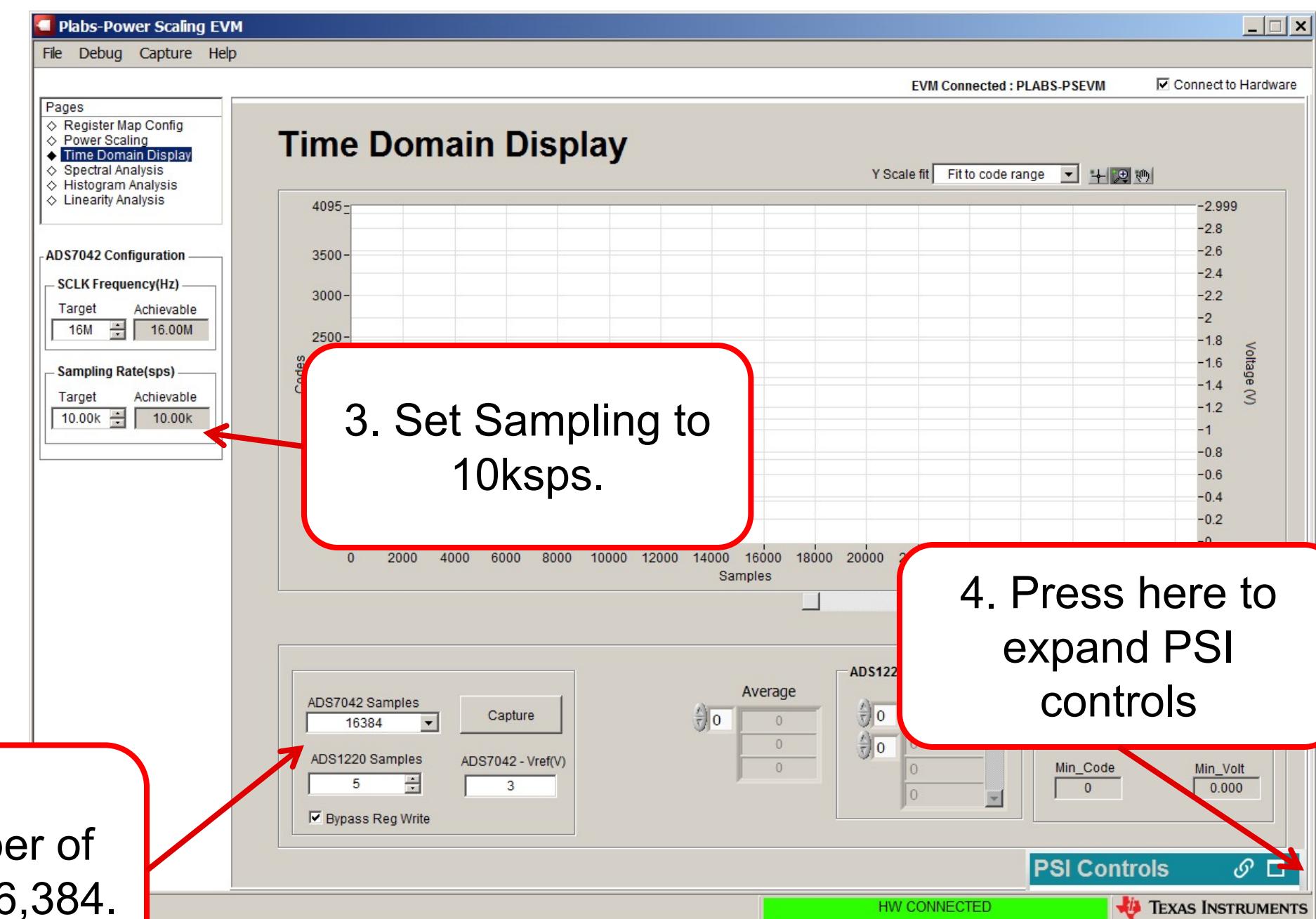

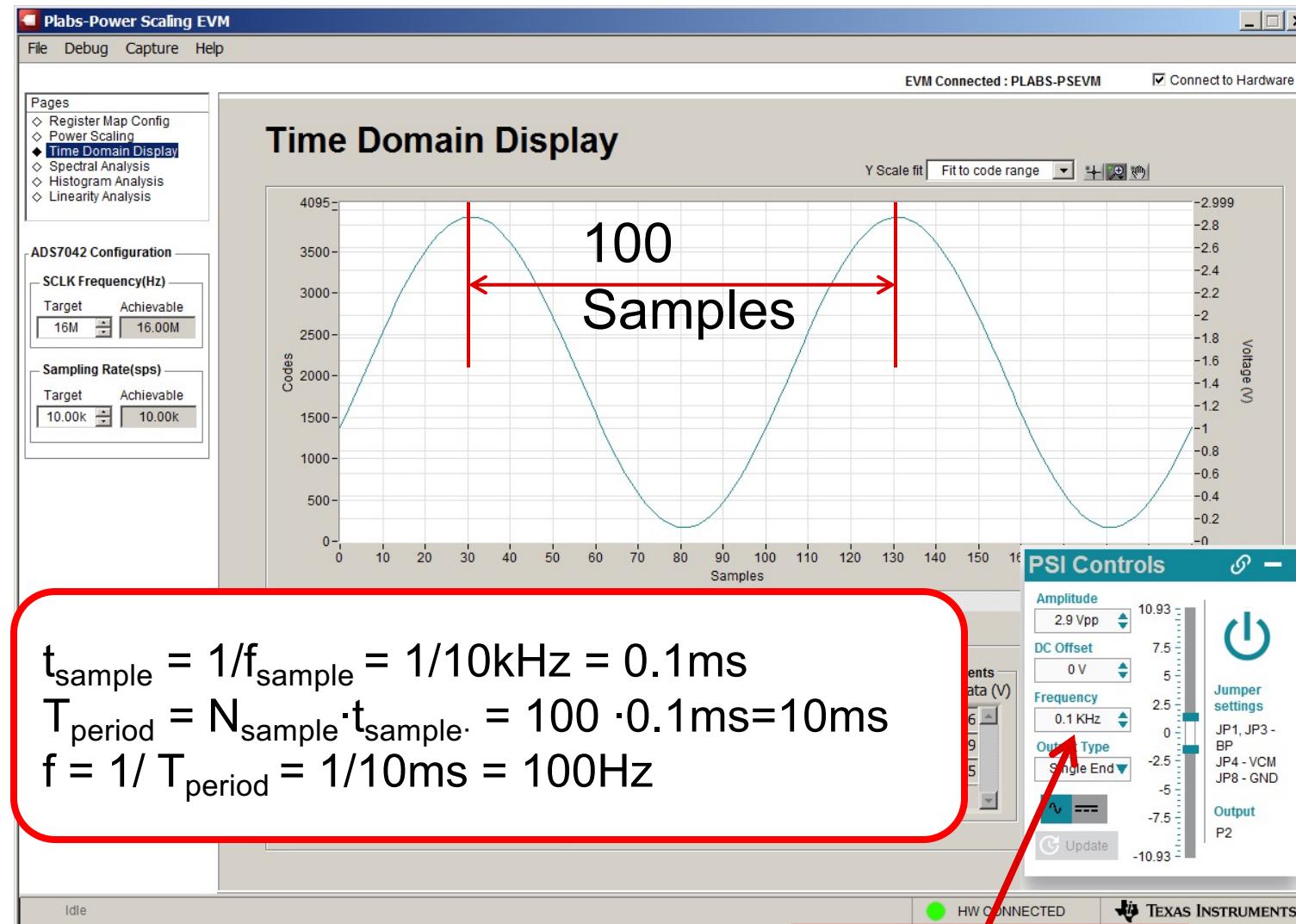Time domain for 0.1kHz and 10.1kHz look the same




$$t_{\text{sample}} = 1/f_{\text{sample}} = 1/10\text{kHz} = 0.1\text{ms}$$

$$T_{\text{period}} = N_{\text{sample}} \cdot t_{\text{sample}} = 100 \cdot 0.1\text{ms} = 10\text{ms}$$


$$f = 1/T_{\text{period}} = 1/10\text{ms} = 100\text{Hz}$$

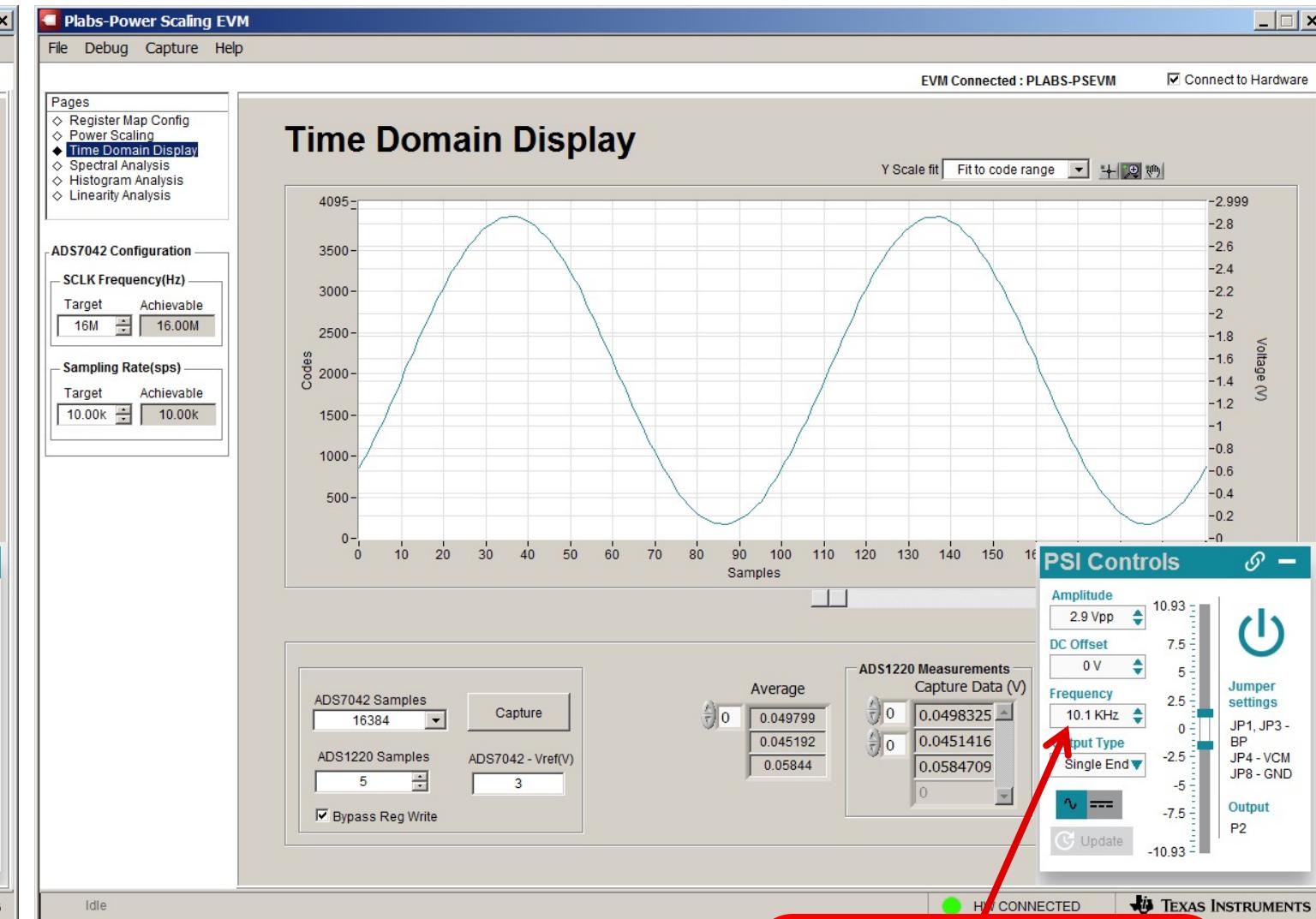f_{input} = 0.1kHz
Vin = 2.9V
Offset = 0V




f_{input} = 10.1kHz
Vin = 2.9V
Offset = 0V

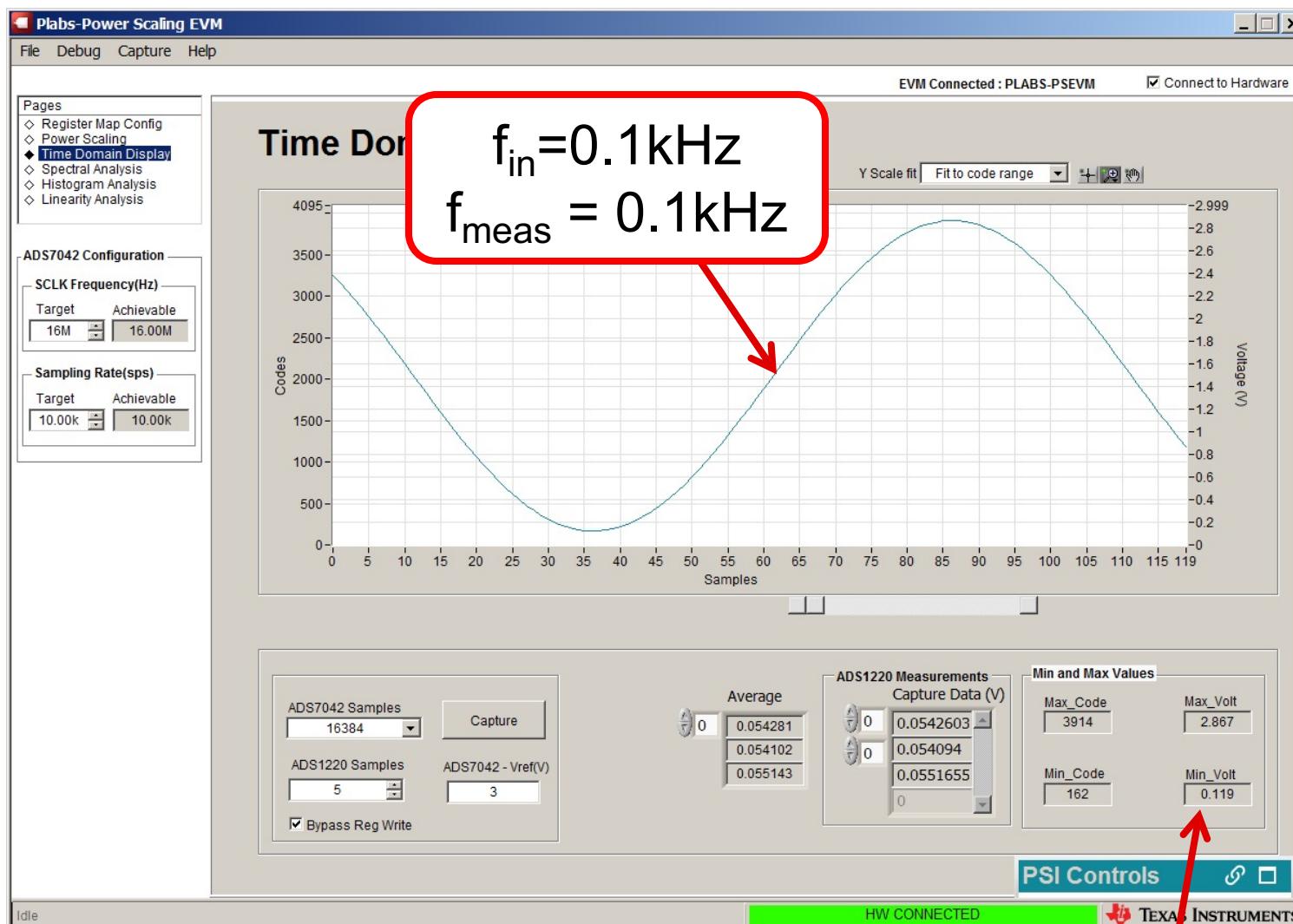Time domain for 0.1kHz and 10.1kHz look the same



$$f_{in} = 0.1\text{kHz}$$

$$f_{meas} = 0.1\text{kHz}$$

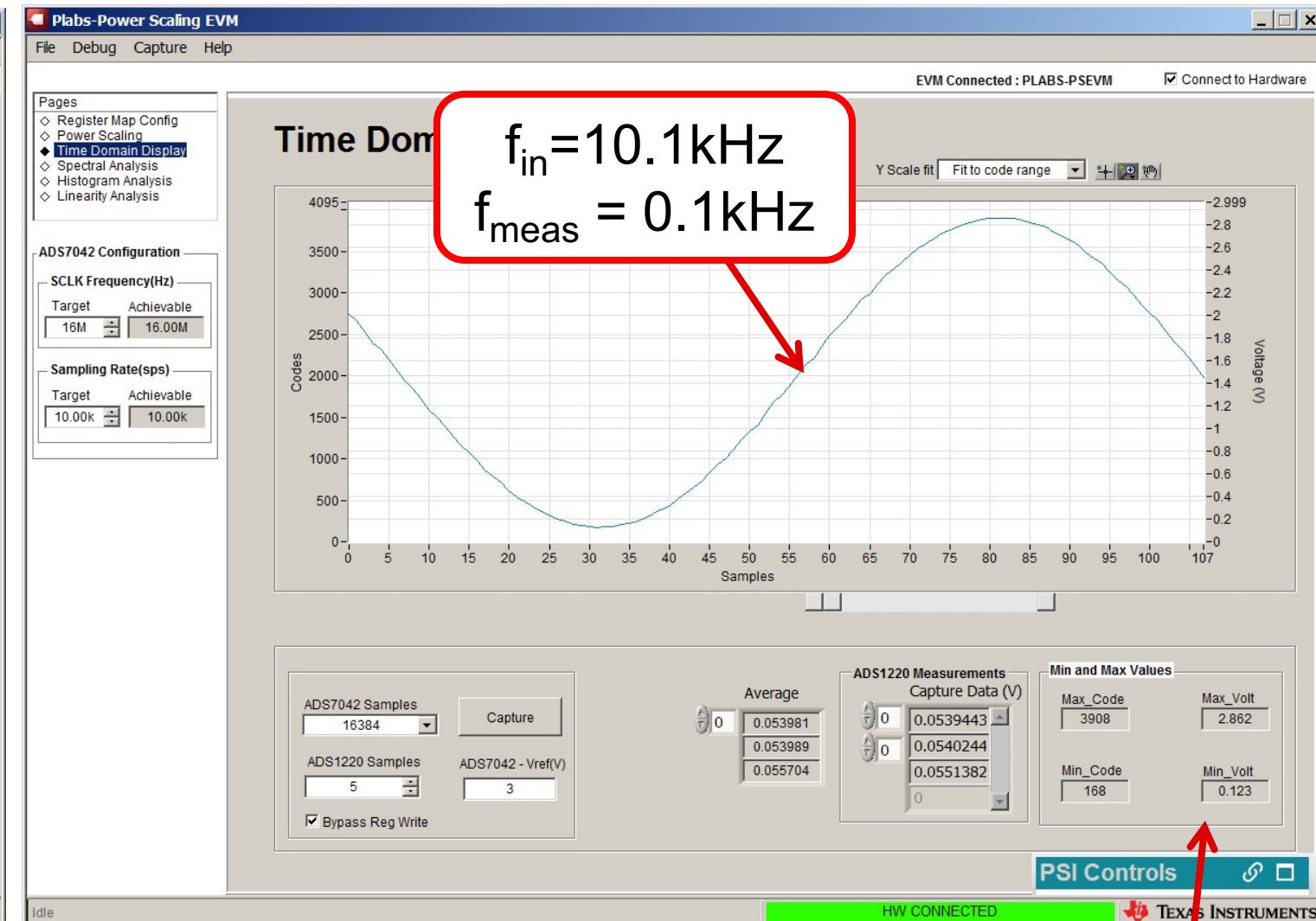


$$f_{in} = 10.1\text{kHz}$$

$$f_{meas} = 0.1\text{kHz}$$


$$V_{pp} = 2.867 - 0.119 = 2.748\text{V}$$

$$V_{pp} = 2.852 - 0.123 = 2.729\text{V}$$

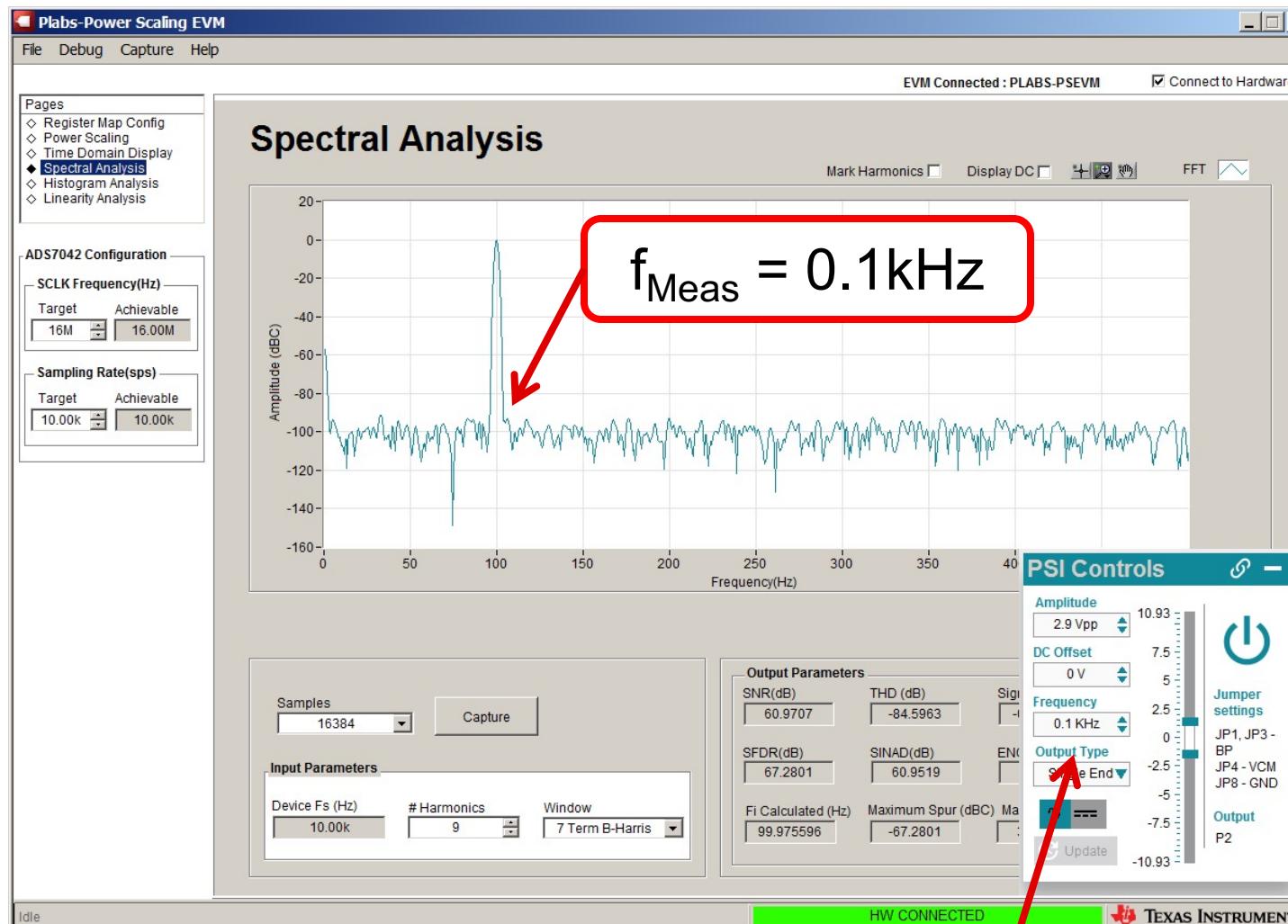Frequency domain for 0.1Hz and 10.1kHz the same




$f_{\text{input}} = 0.1\text{kHz}$

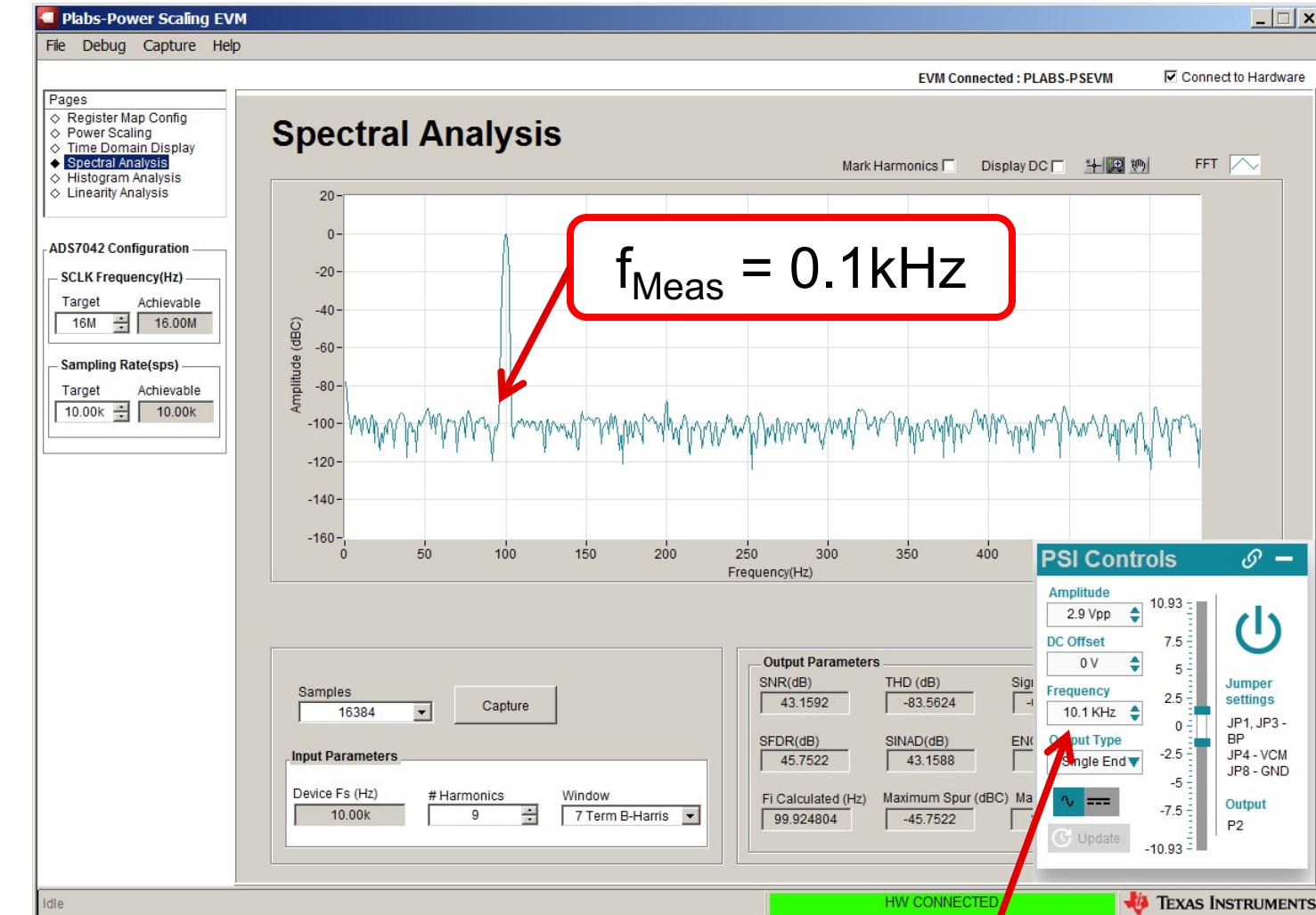


$f_{\text{input}} = 10.1\text{kHz}$


Install the Sallen Key Filter

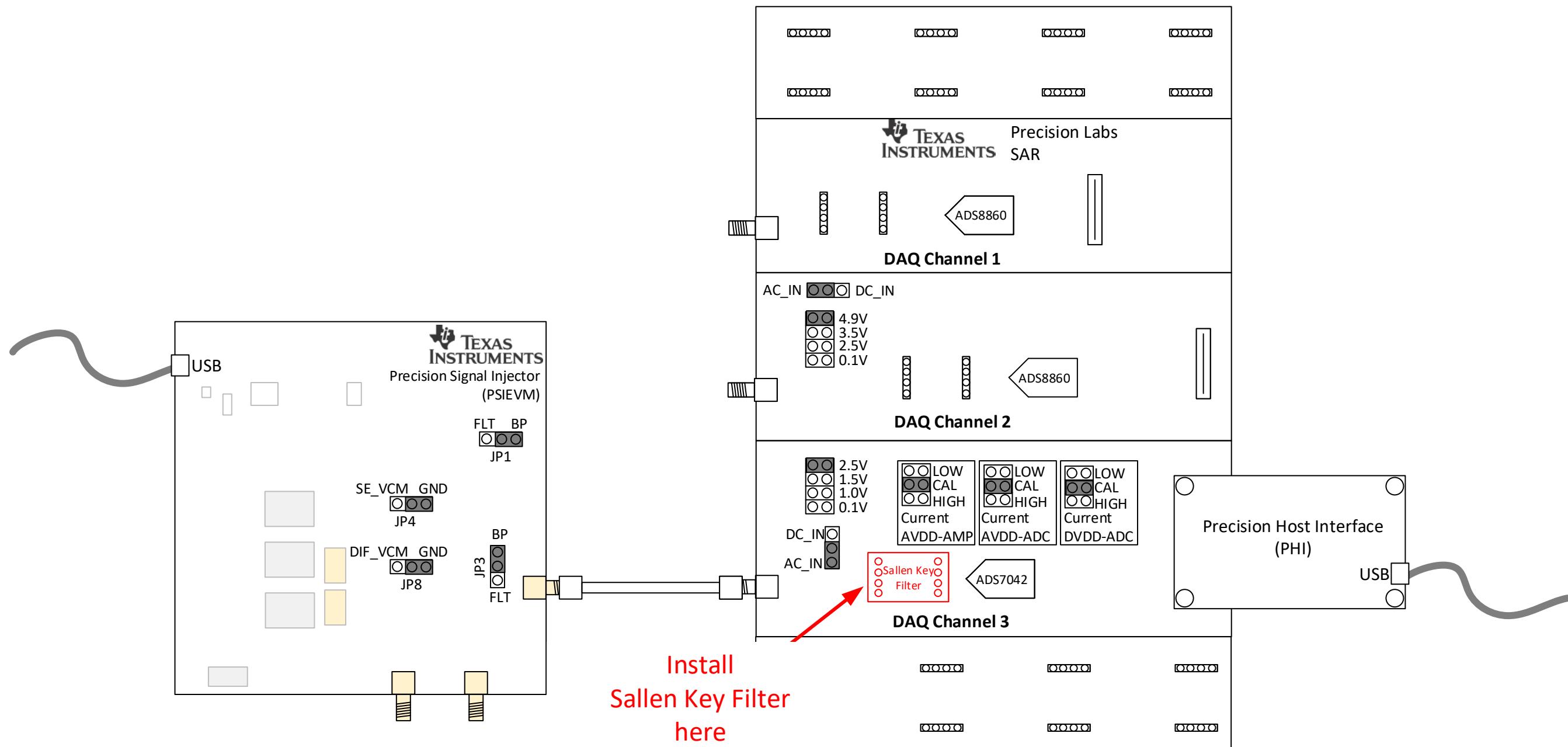

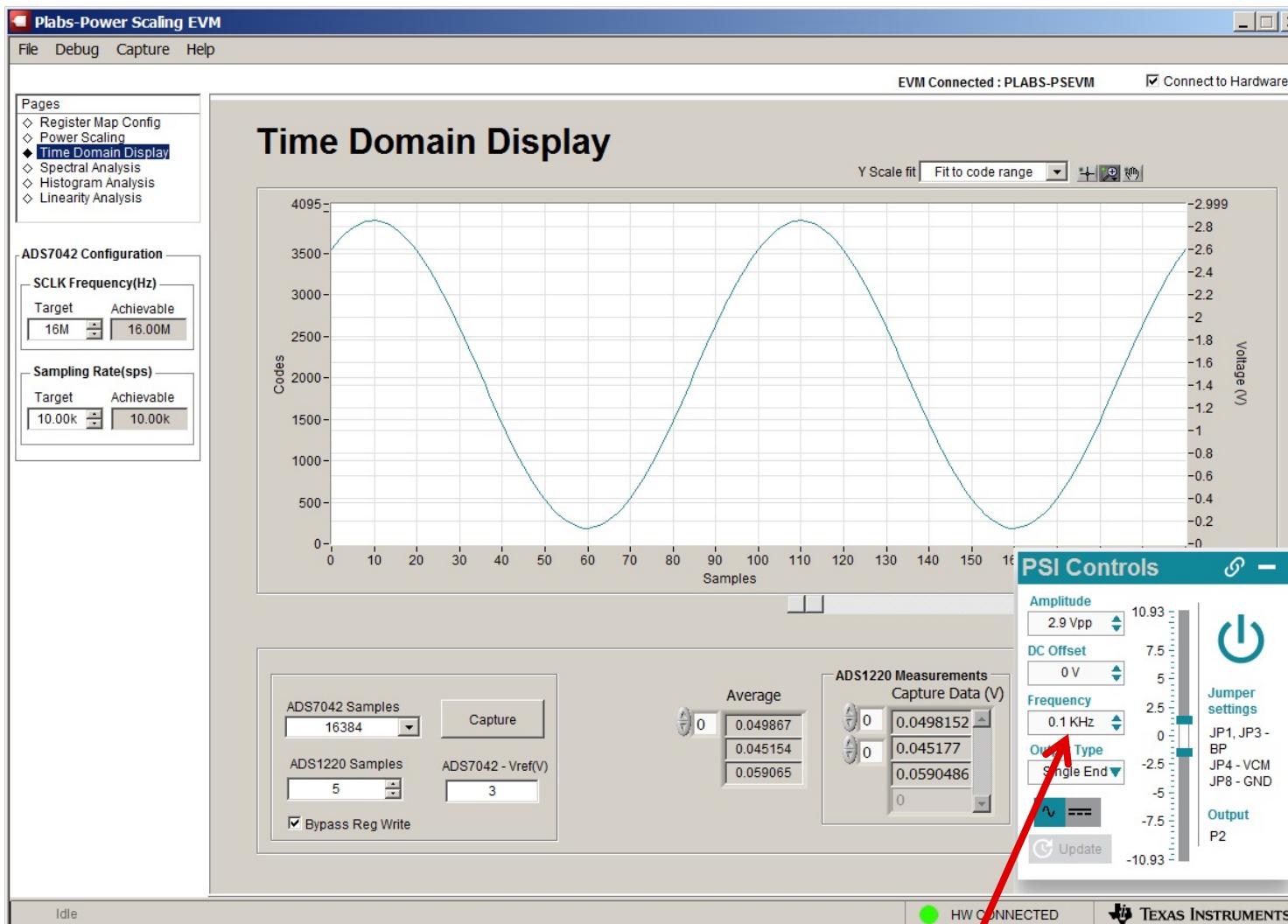Antialiasing filter with 0.1kHz and 10.1kHz Input




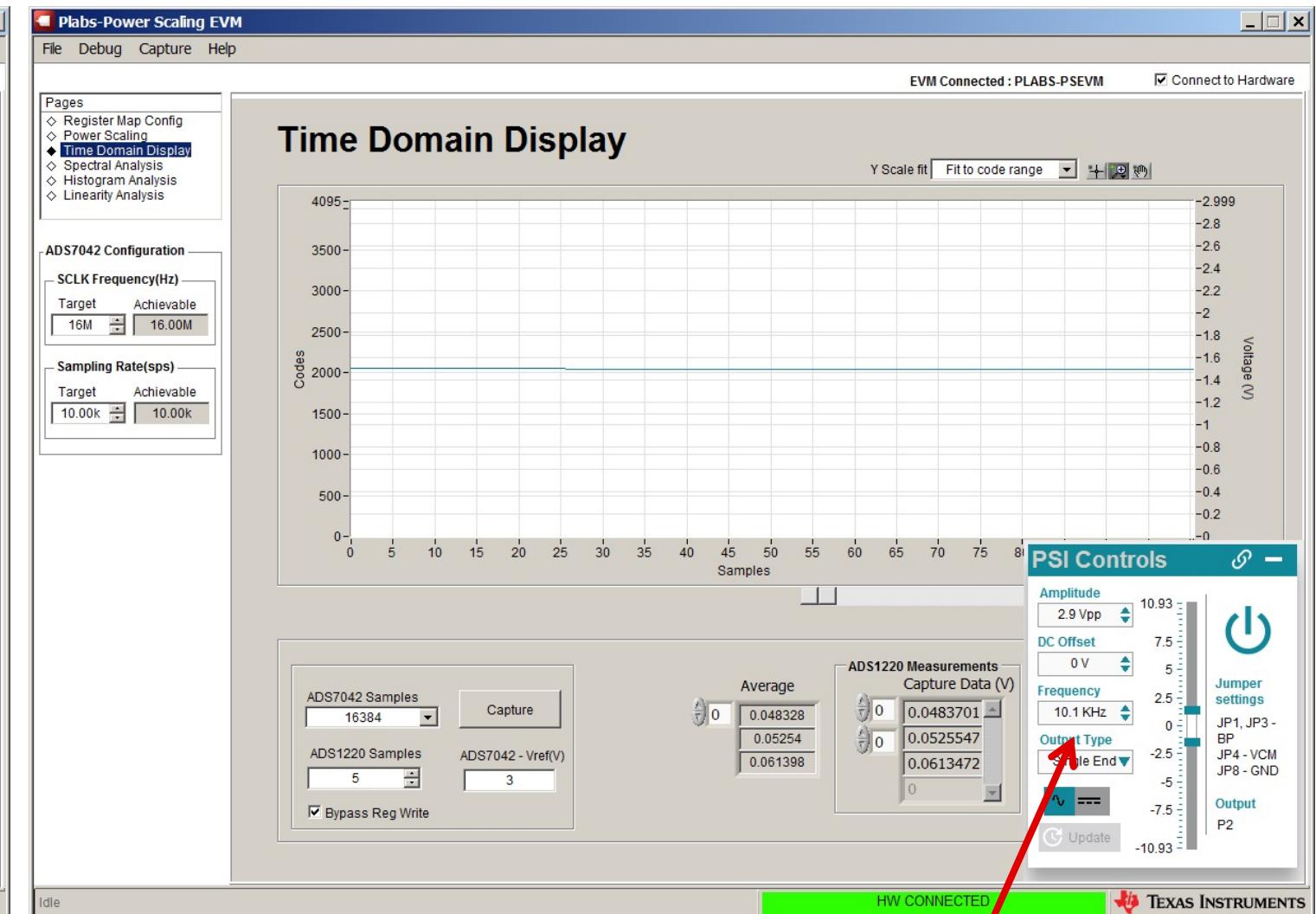$f_{\text{input}} = 0.1\text{kHz}$
 $V_{\text{in}} = 2.9\text{V}$
Offset = 0V




$f_{\text{input}} = 10.1\text{kHz}$
 $V_{\text{in}} = 2.9\text{V}$
Offset = 0V

Zoom in on Alias

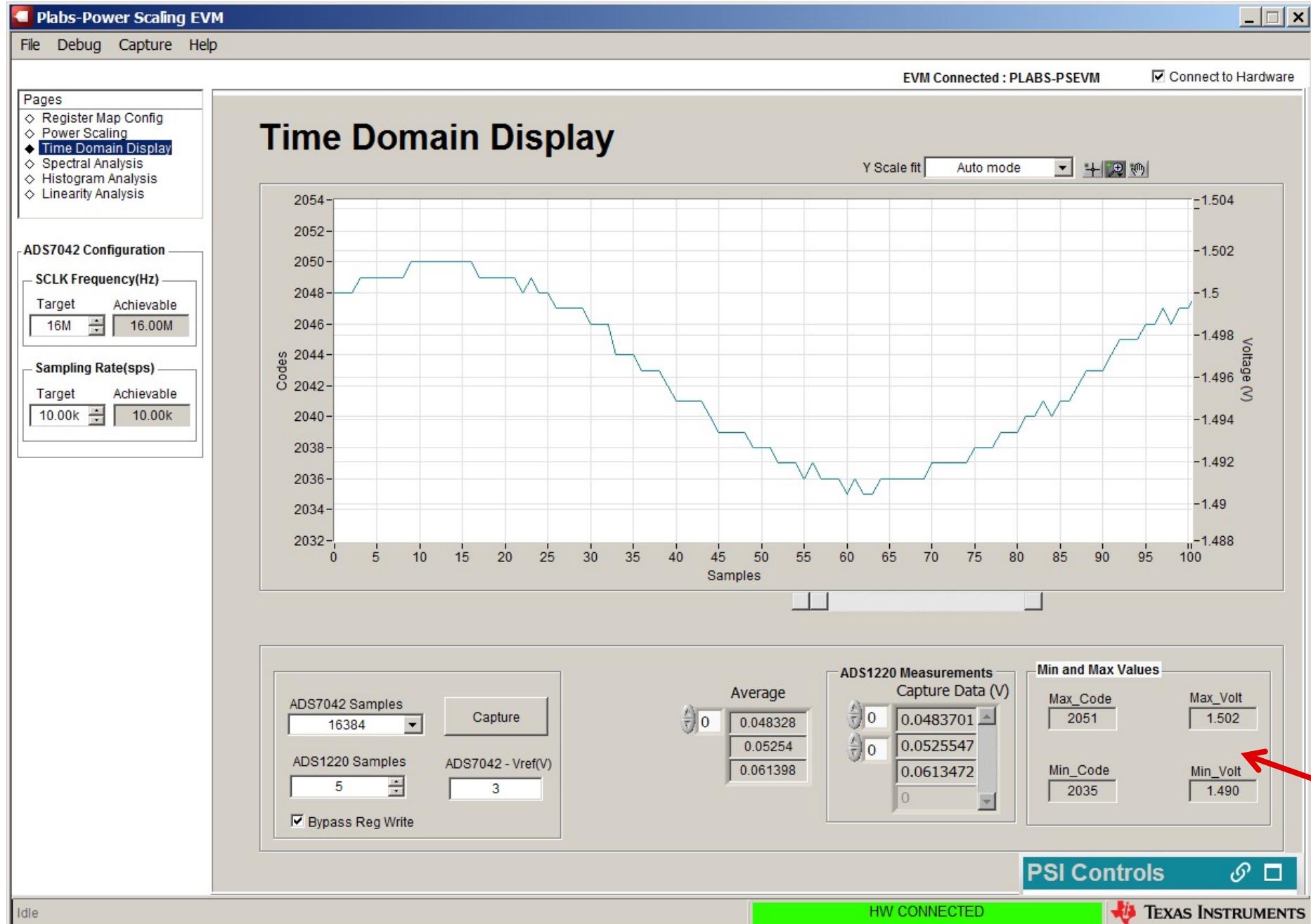

Simulated Result

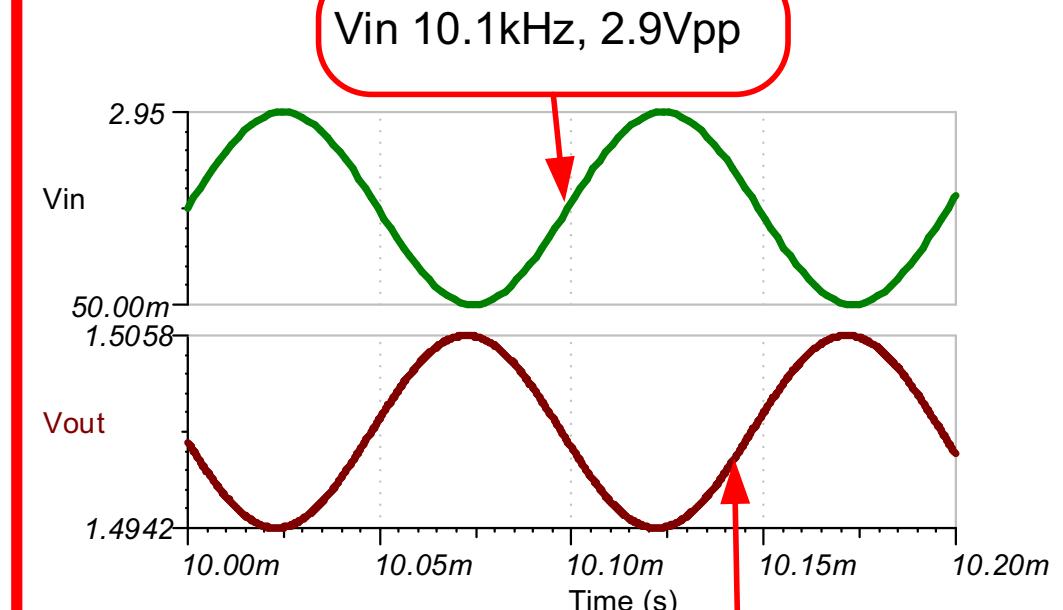

Vout 10.1kHz, 11.6mVpp

$$V_{pp} = 1.502 - 1.490 = 0.012V$$


Measured vs Expected Results

$f_{\text{ samp}} = 10\text{kHz}$

Your results should show the same trend as the expected result but the specific values will differ.

Device		Expected		Example Measurements		Your Measurements			
	Device	f_{in} (kHz)	V_{in} (V)	f_{meas} (kHz)	V_{adc} (Vpp)	f_{meas} (kHz)	V_{adc} (Vpp)	f_{meas} (kHz)	V_{adc} (Vpp)
1	OPA320 Good filter2	0.1	2.9	0.1	2.9	0.1	2.748		
2	OPA320 Good filter2	10.1	2.9	0.1	2.9	0.1	2.729		
3	Sallen-Key	0.1	2.9	0.1	2.9	0.1	2.711		
4	Sallen-Key	10.1	2.9	0.1	11.6m	0.1	12m		
5	Sallen-Key (test design)	5.1	0.02	4.9	0.0				
6	Sallen-Key (test design)	5.1	2.9	4.9	44.4m				

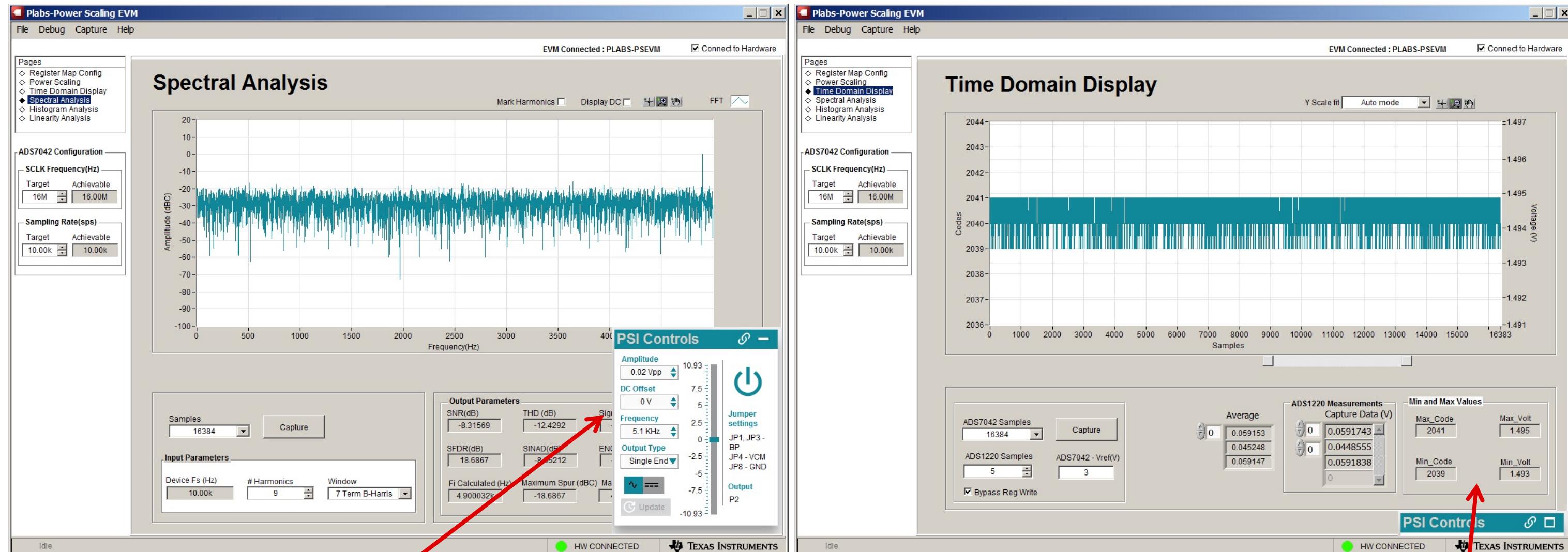Check Antialiasing Filter Near Nyquist ($V_{in} = 20mV$)




$f_{input} = 5.1\text{kHz}$
 $V_{in} = 0.02\text{V}$
Offset = 0V

Expected Output at 5.1kHz


$$V_{out} = (20mV) \cdot \left(10^{\left(\frac{-36.1\text{dB}}{20} \right)} \right) = 313\mu\text{V}$$

$$V_{pp} = 1.495 - 1.493 = 2\text{mV}$$

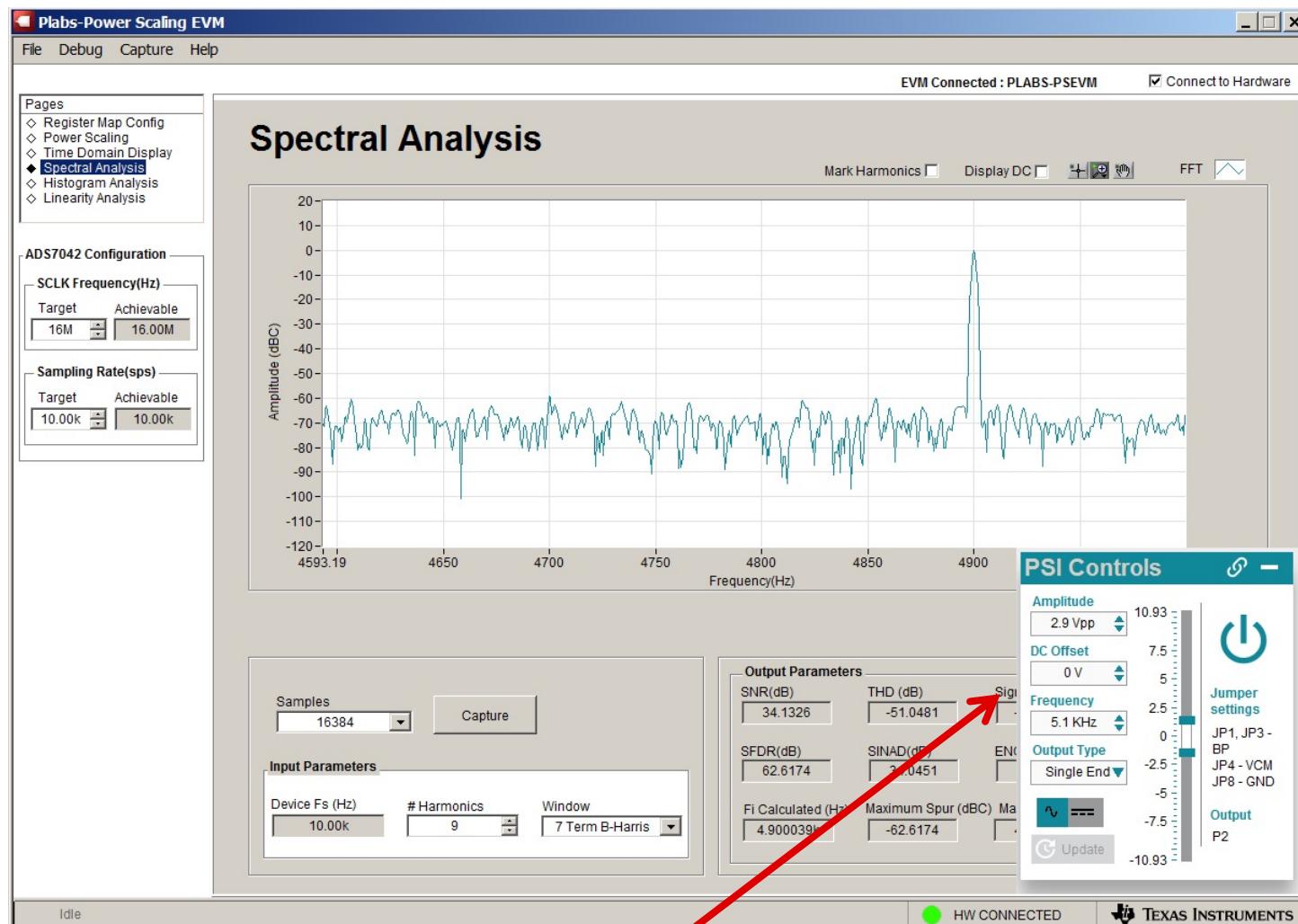Check Antialiasing Filter Near Nyquist (Vin = 2.9V)



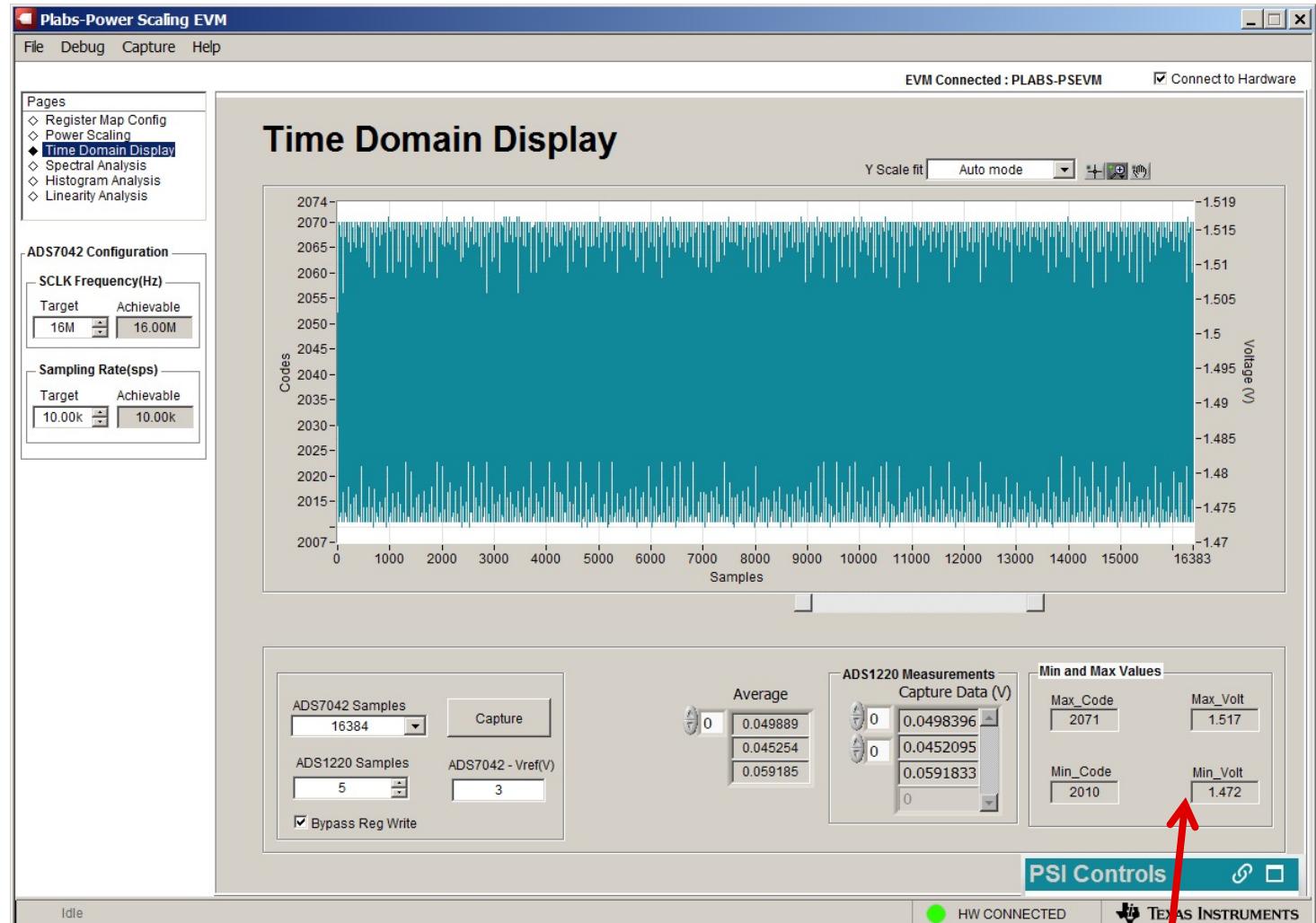$f_{\text{input}} = 5.1\text{kHz}$
 $V_{\text{in}} = 2.9\text{V}$
Offset = 0V



Expected Output at 5.1kHz
 $V_{\text{out}} = (2.9V) \cdot \left(10^{\frac{(-36.1\text{dB})}{20}} \right) = 45.4\text{mV}$

$V_{\text{pp}} = 1.517 - 1.472 = 0.045\text{V}$

Measured vs Expected Results

$f_{\text{ samp}} = 10\text{kHz}$

Your results should show the same trend as the expected result but the specific values will differ.

Device		Expected		Example Measurements		Your Measurements			
	Device	f_{in} (kHz)	V_{in} (V)	f_{meas} (kHz)	V_{adc} (Vpp)	f_{meas} (kHz)	V_{adc} (Vpp)	f_{meas} (kHz)	V_{adc} (Vpp)
1	OPA320 Good filter2	0.1	2.9	0.1	2.9	0.1	2.748		
2	OPA320 Good filter2	10.1	2.9	0.1	2.9	0.1	2.729		
3	Sallen-Key	0.1	2.9	0.1	2.9	0.1	2.711		
4	Sallen-Key	10.1	2.9	0.1	11.6m	0.1	12m		
5	Sallen-Key (test design)	5.1	0.02	4.9	0.0	-na-	2m		
6	Sallen-Key (test design)	5.1	2.9	4.9	44.4m	4.9	45m		

Thanks for your time!