


# PLL Building Blocks Part 1

## TI Precision Labs – Clocks and Timing


Presented by Dean Banerjee

Prepared by Liam Keese


# Phase lock loop (PLL) block diagram

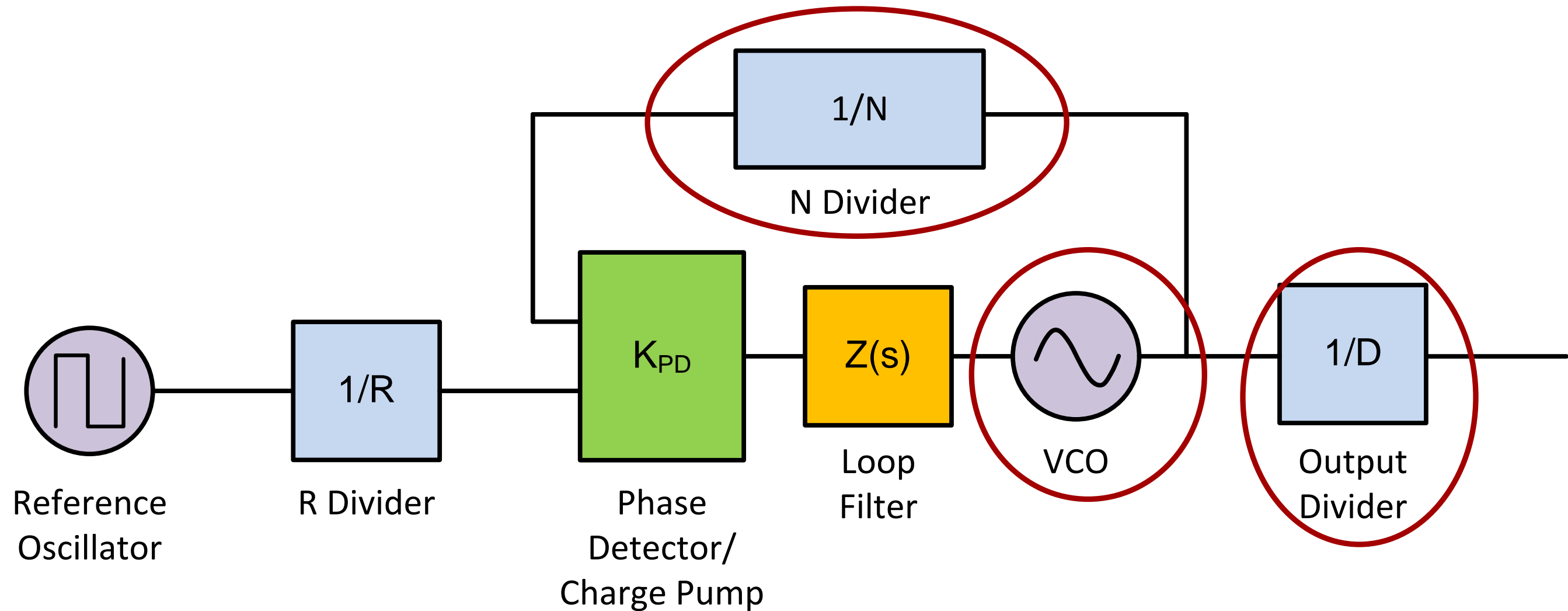

# Voltage controlled oscillator (VCO)

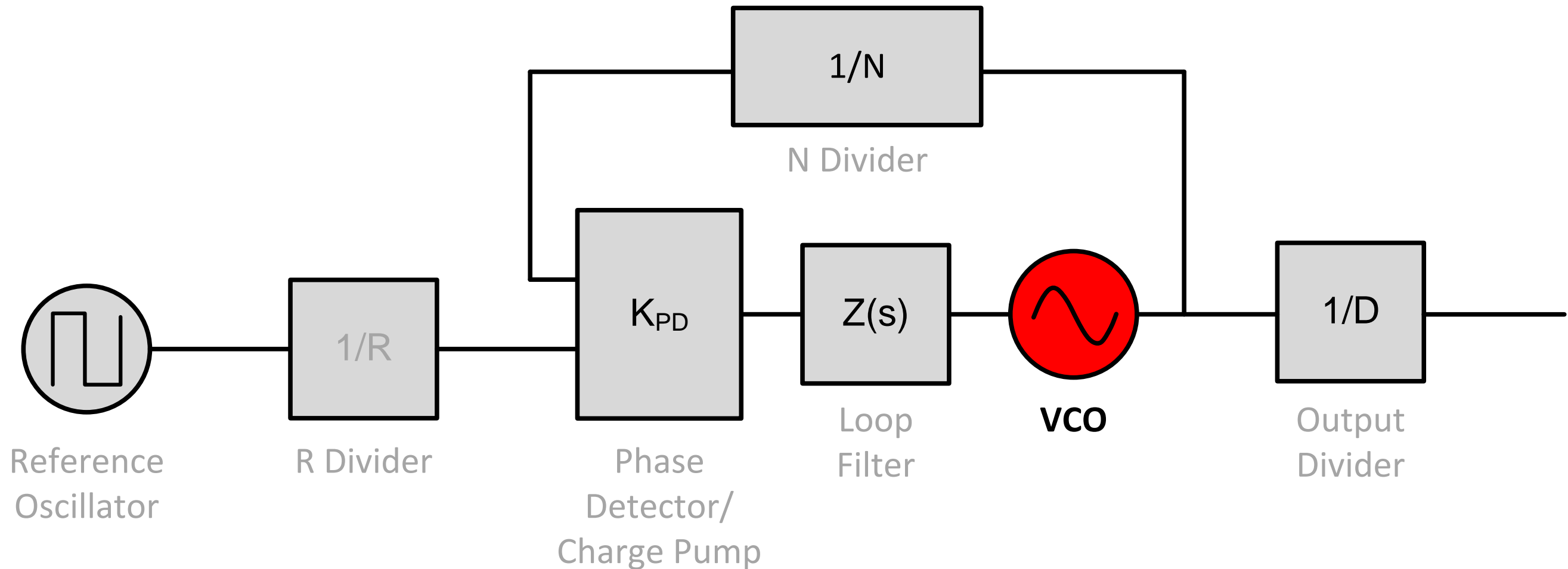


# VCO resonator

 

$$f = \frac{1}{2\pi\sqrt{L \cdot C}}$$

 
f = resonant frequency  
L = inductance  
C = capacitance



$$\tau = 2\pi\sqrt{\frac{L}{g}}$$


Tau = period  
L = length of the pendulum  
g = acceleration due to gravity

# The real-world inductor

 


$$Q_L(f) = \frac{X_L}{R_L} = \frac{2\pi \cdot f \cdot L}{R}$$

# Now add the stimulus

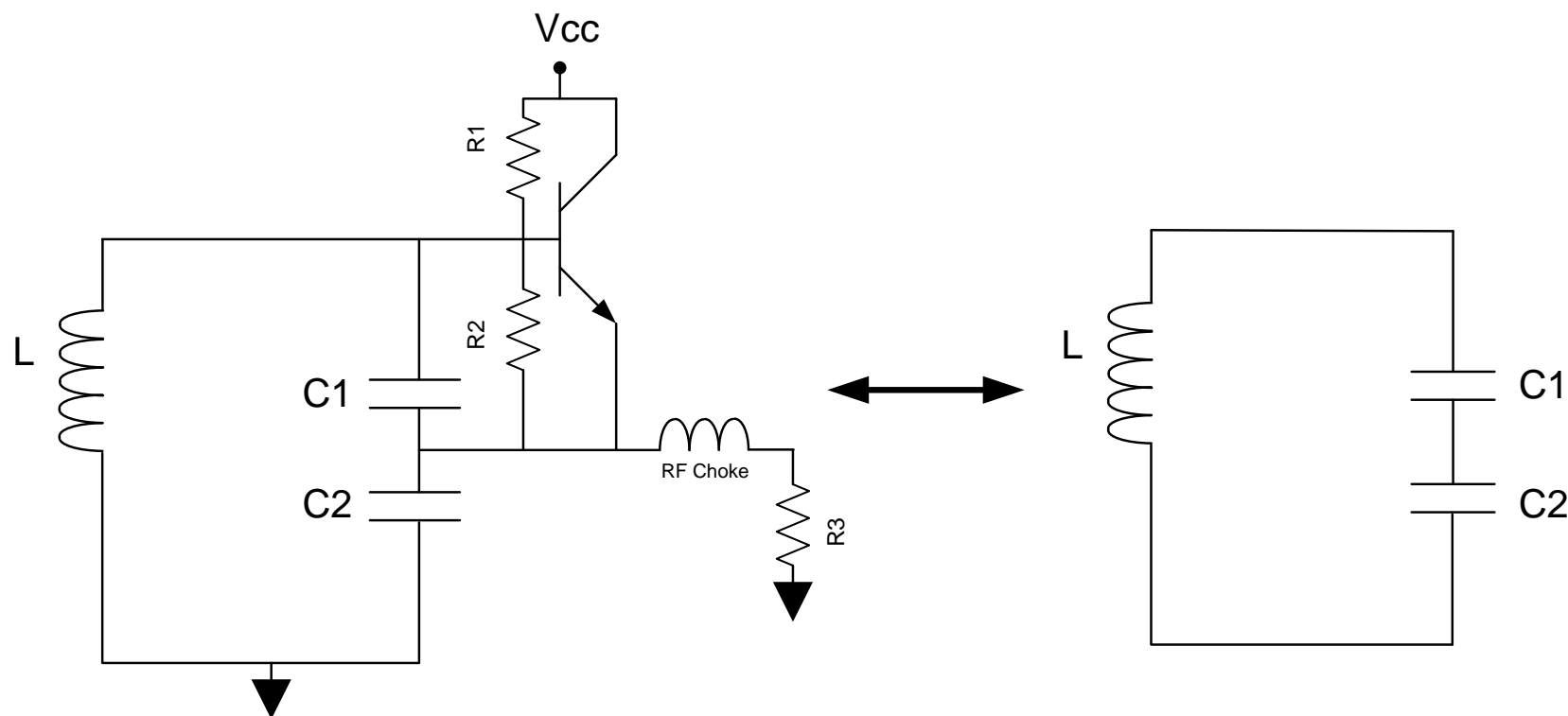

**Amplified signal from emitter is lightly coupled into the circuit to sustain oscillation**



# Example VCO circuit

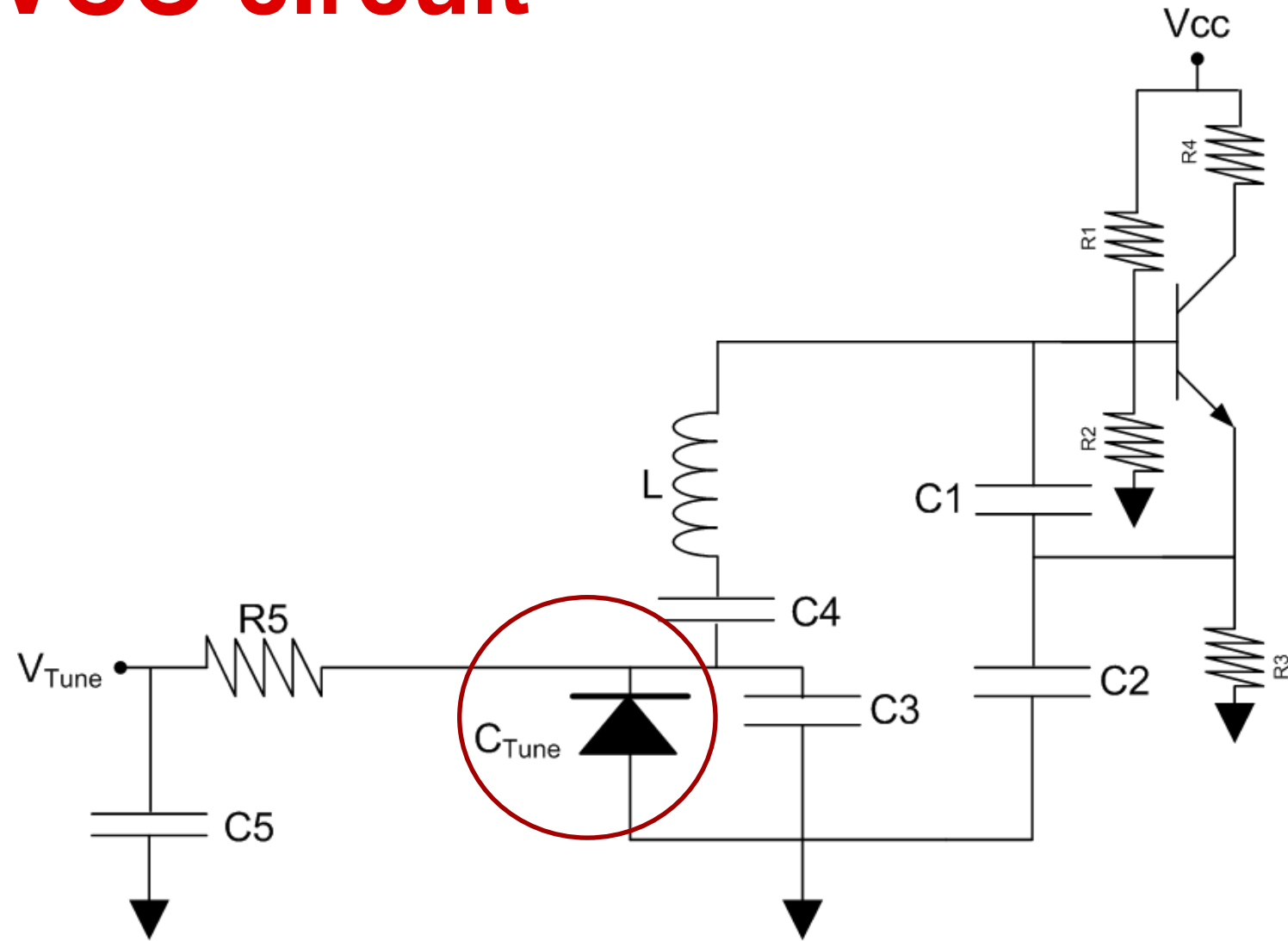




# VCO tuning range

## Switched Capacitor Bank

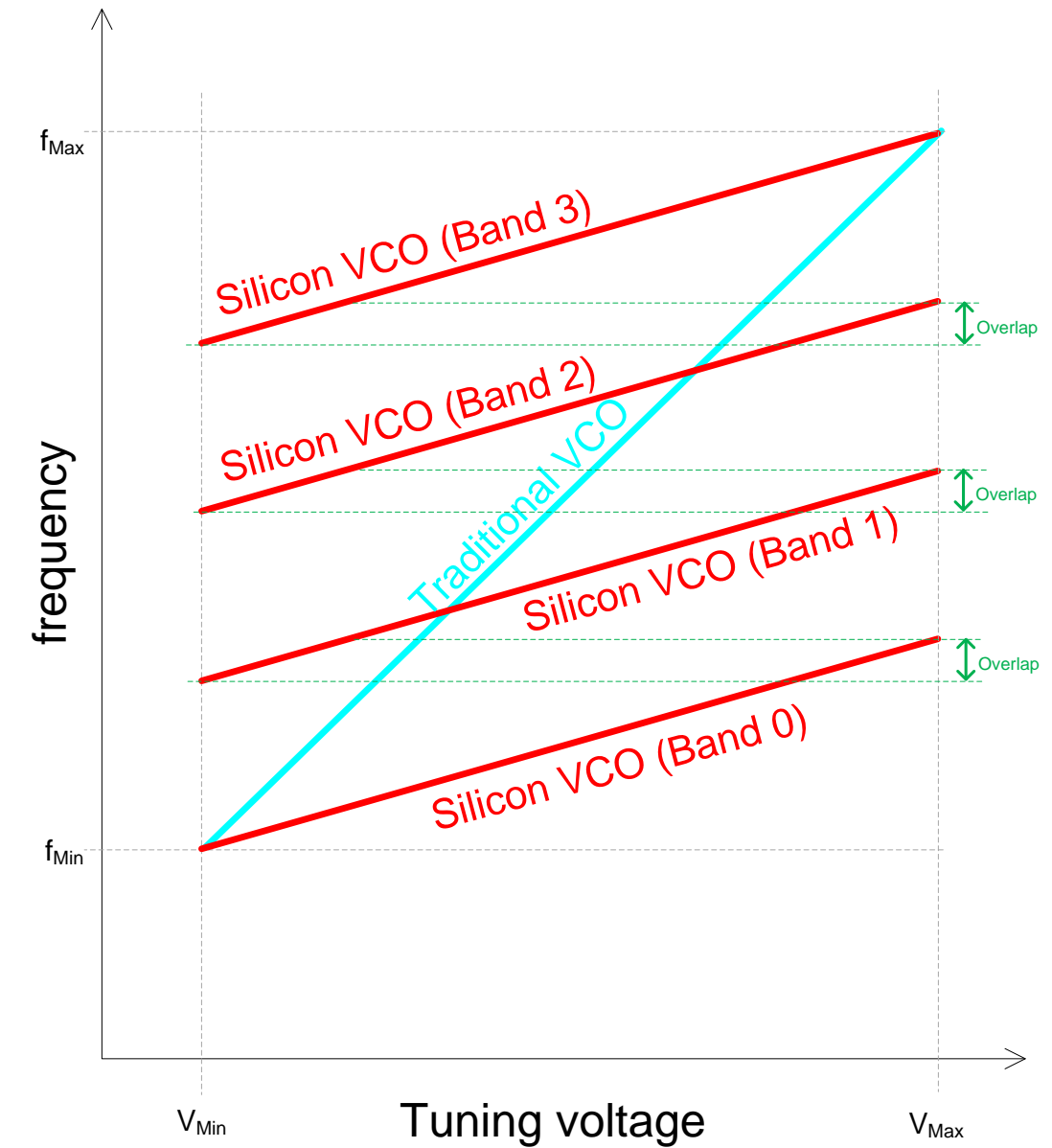 




# Phase lock loop overview

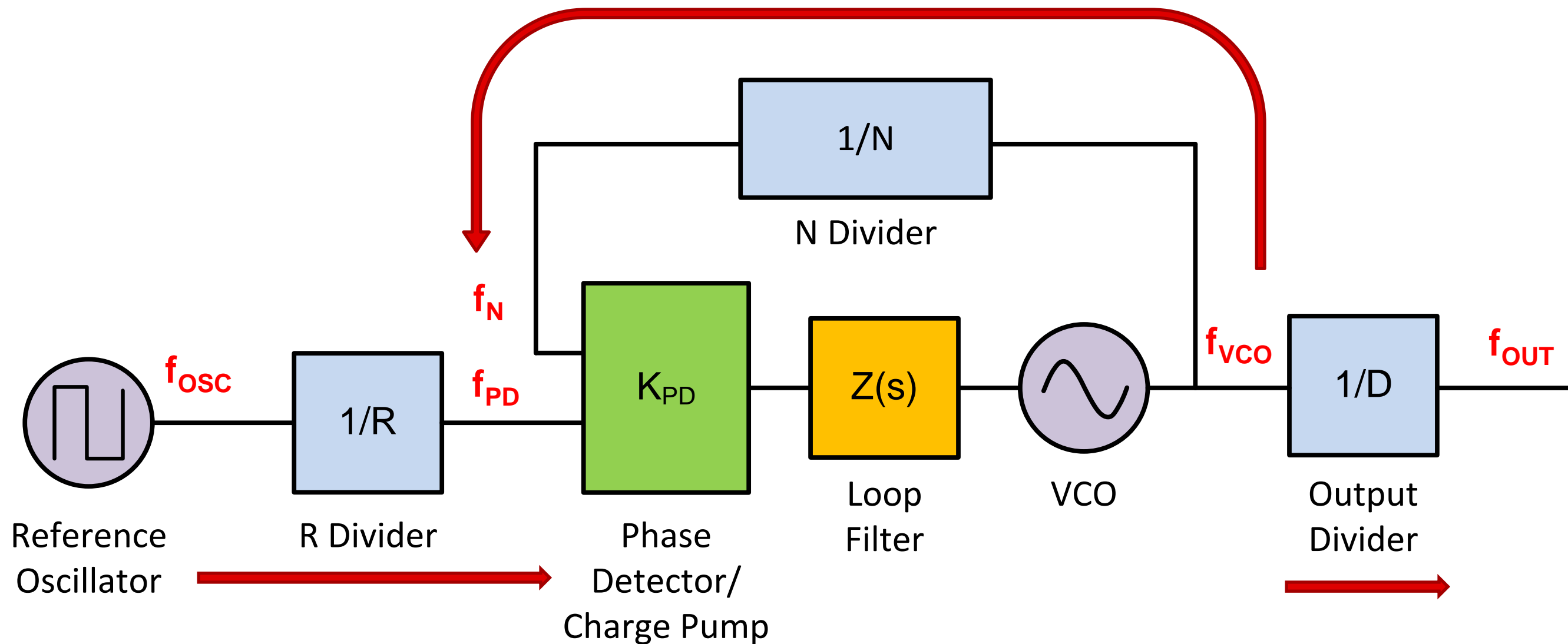

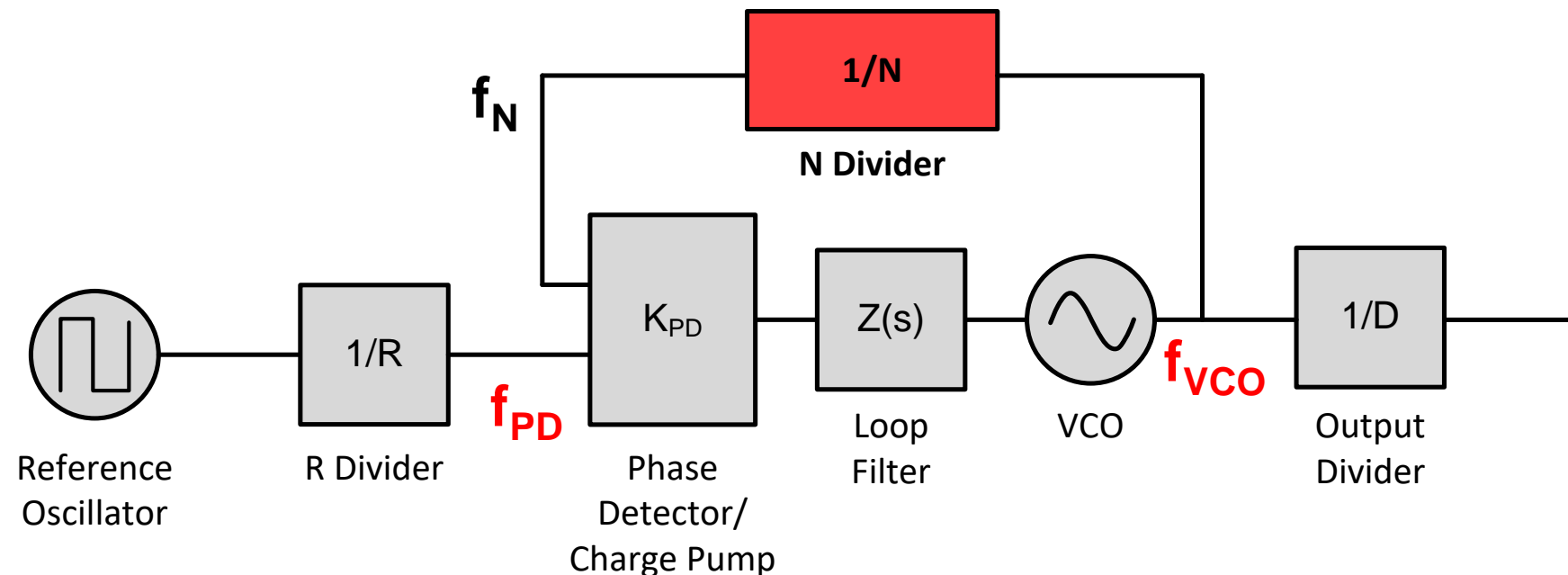
# High-frequency feedback (N) divider

- N counter value
  - $N = f_{VCO}/f_N = f_{VCO}/f_{PD}$
- Input to this counter can be high frequency
- Prescalers are typically inside this counter




# High frequency feedback (N) divider

## Single Modulus Prescaler

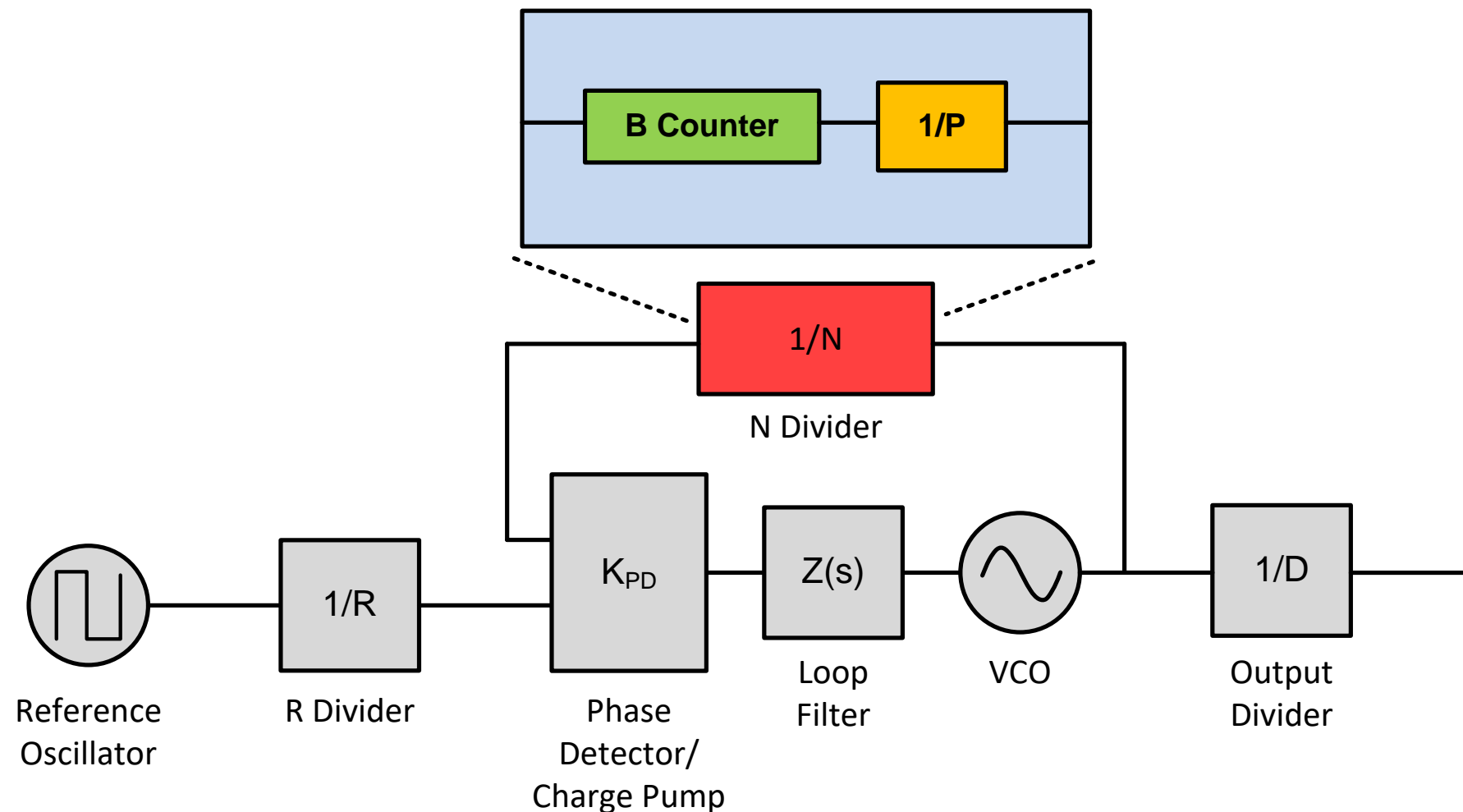

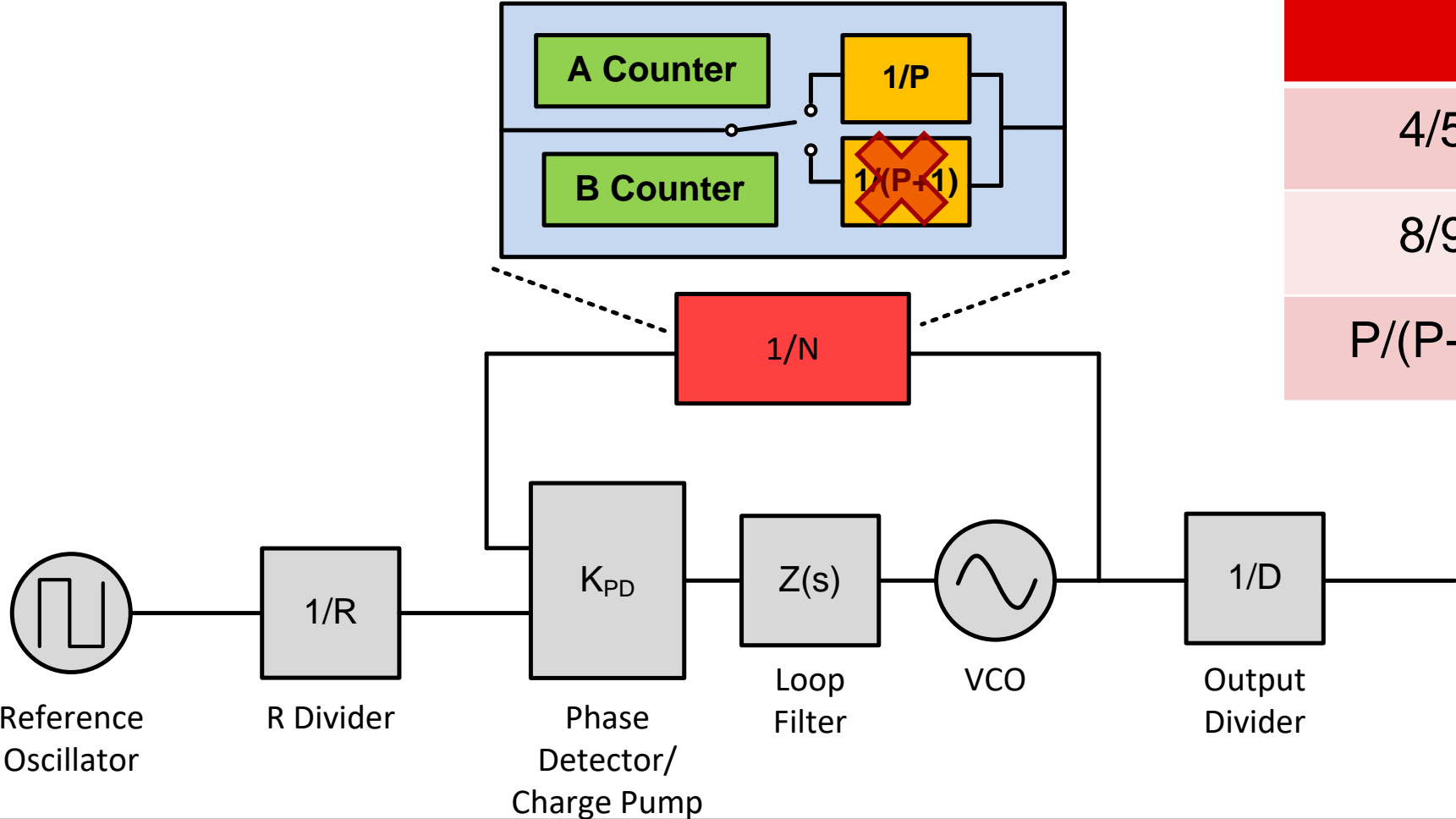
# High-frequency feedback (N) divider

- Dual modulus prescaler
  - $N = A \times (P+1) + (B-A) \times P = P \times B + A$



Prescaler	Minimum Continuous Divide
4/5	12
8/9	56
$P/(P+1)$	$P \times (P-1)$

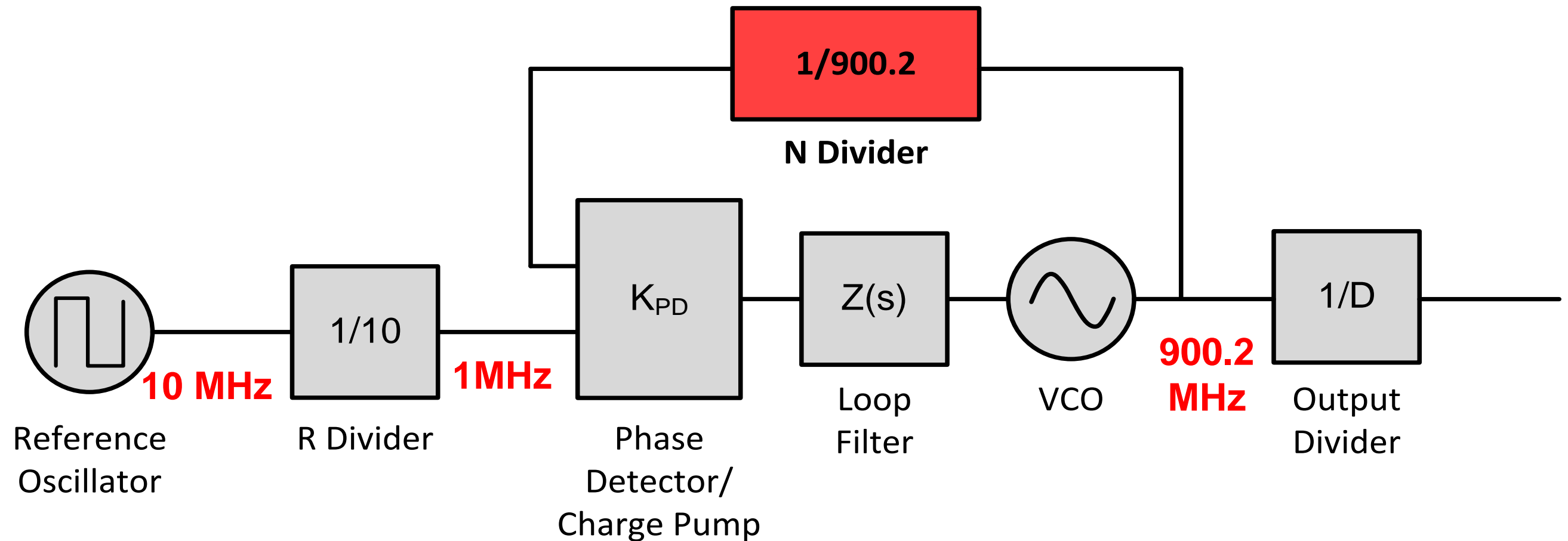
# Fractional dividers (Simple 1st order modulator)




# Fractional dividers (Simple 1st order modulator)

## Fractional divide timing error

Phase Detector Cycle	Accumulator (Cycles)	N Value	Time for Rising Edge for Dividers (ns)	
			Actual	Desired
1	0.2	900	999.7778	1000
2	0.4	900	1999.5557	2000
3	0.6	900	2999.3335	3000
4	0.8	900	3999.1113	4000
5	0	901	5000.0000	5000

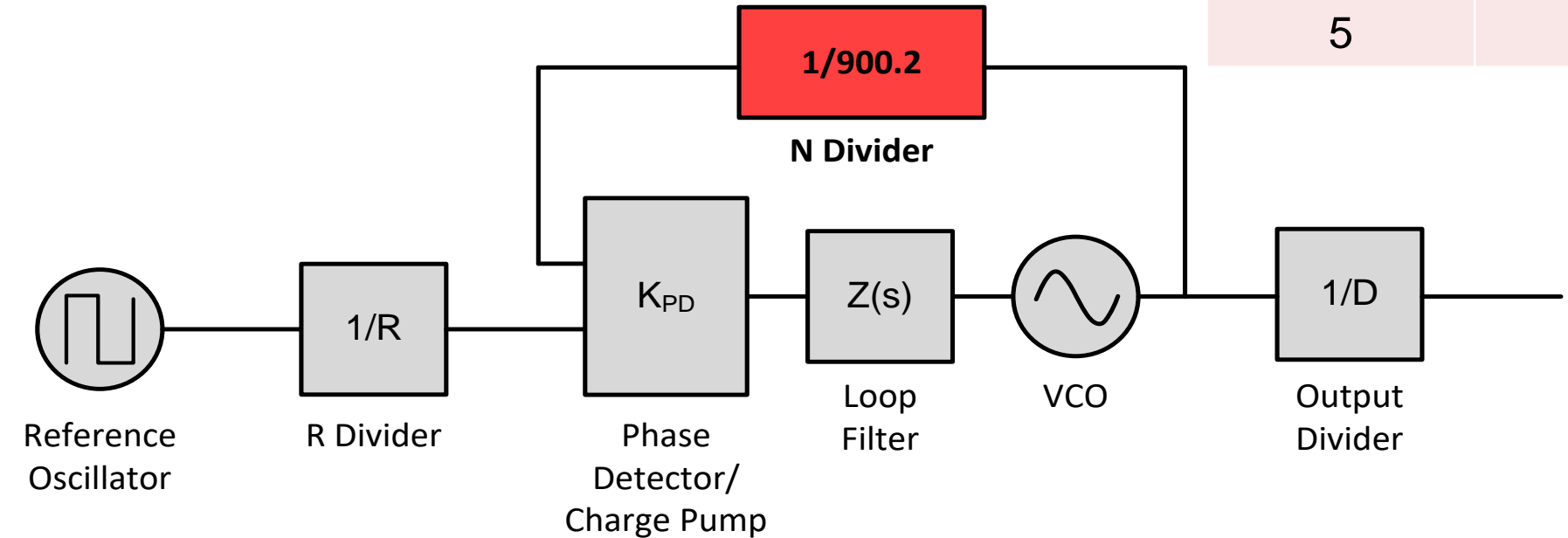

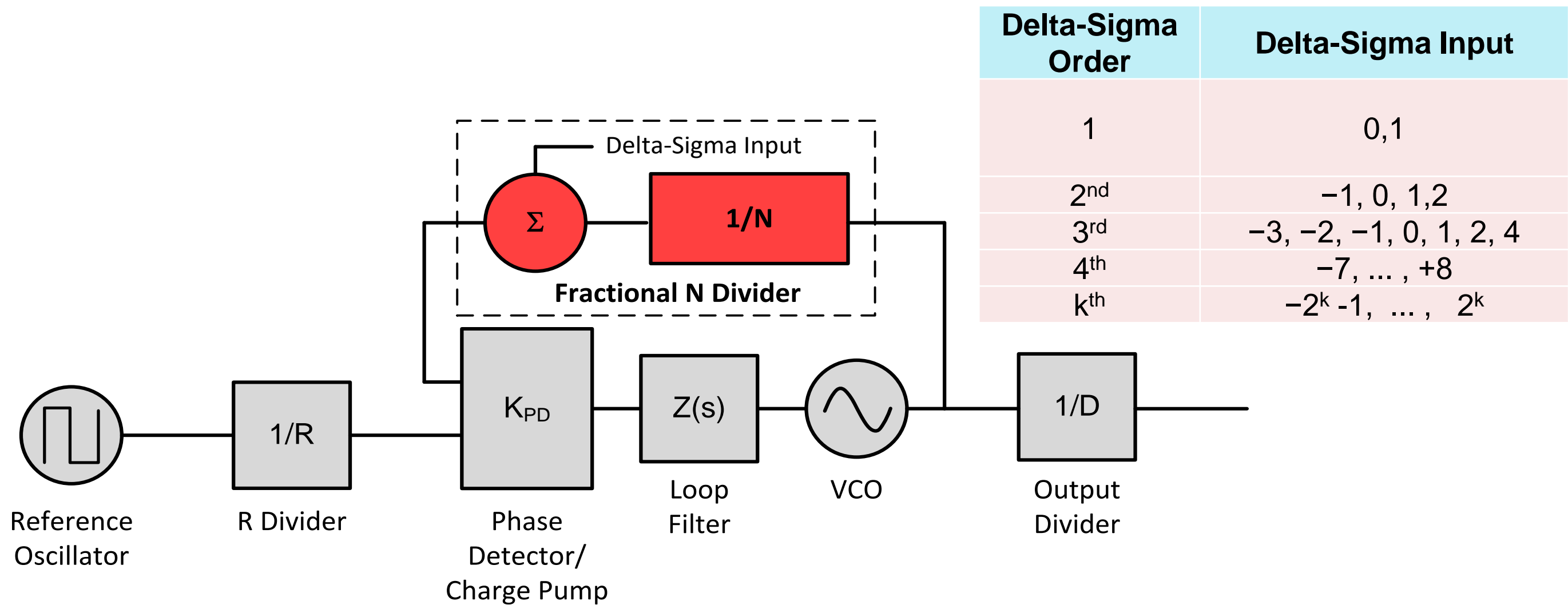
# Fractional dividers (High-order modulators)






# Fractional dividers performance ( $f_{PD} = 10\text{ MHz}$ )

## Spur and Fractional Noise Shaping

 

## Spur Example for fraction of 1/10

 

**To find more clocks and timing technical  
resources and search products, visit  
[ti.com/clocks](https://ti.com/clocks)**

# Short Quiz

## 1. True or False:

The relationship between  $f_{VCO}$  (VCO frequency),  $f_{PD}$  (phase detector frequency),  $f_n$  (N divider output frequency) is  $f_{VCO}/f_N = f_{VCO}/f_{PD} = N$

# Short Quiz

## 1. True or False:

The relationship between  $f_{VCO}$  (VCO frequency),  $f_{PD}$  (phase detector frequency),  $f_n$  (N divider output frequency) is  $f_{VCO}/f_N = f_{VCO}/f_{PD} = N$

# Short Quiz

## 2. Choose one:

Which techniques can be used to increase VCO tuning range?

- (a) Fractional N divider
- (b) Switchable capacitor or inductor array
- (c) Output divider

# Short Quiz

## 2. Choose one:

Which techniques can be used to increase VCO tuning range

(a) Fractional N divider

(b) Switchable capacitor or inductor array

(c) Output divider

# Short Quiz

## 3. True or False:

A fractional N modulator decreases the noise generated at higher frequencies.



# Short Quiz

## 3. True or False:

A fractional N modulator decreases the noise generated at higher frequencies

# Short Quiz

## 4. Choose all that apply:

Which of below statements apply when using a dual modulus prescaler?

- a) Counter will divide by  $(P+1)$  A times
- b)  $B < A$
- c)  $N = P \times B + A$

# Short Quiz

## 4. Choose all that apply:

Which of below statements apply when using a dual modulus prescaler?

a) Counter will divide by  $(P+1)$  A times

b)  $B < A$

c)  $N = P \times B + A$



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)